

1/15/24

Welcome to
ECE 3050

①

Formatting Guide

* Engineering Notation

$$10^{-3} = \text{milli} [\text{m}]$$

$$10^{-6} = \text{micro} [\mu]$$

$$10^{-9} = \text{nano} [\text{n}]$$

$$10^{-12} = \text{pico} [\text{p}]$$

$$10^3 = \text{kilo} [\text{k}]$$

$$10^6 = \text{Mega} [\text{M}]$$

$$10^9 = \text{Giga} [\text{G}]$$

$$10^{12} = \text{Tera} [\text{T}]$$

$$\cancel{0.001} \text{ A} = \boxed{1 \text{ mA}} \cdot \cancel{0.000000002} = \boxed{2 \text{ nF}}$$

* Final Answers

- Must be circled/boxed/double underline

- No fractions, answers in decimal form

$$\text{Ex: } \frac{22 \times 10^{-3} \cancel{\text{E}}}{5 \times 10^{-6} \cancel{\text{F}}} \text{ F}$$

$$\boxed{455.804 \text{ nF}} \\ \boxed{0.456 \mu\text{F}}$$

✓

✓

* Plots


- All axis must be labeled with units

- Plots must title

- Minimum of 4 points

My Plot / Capacitor C. Ringdown

$$f(x) = V_0 e^{-\frac{t}{\tau}}$$

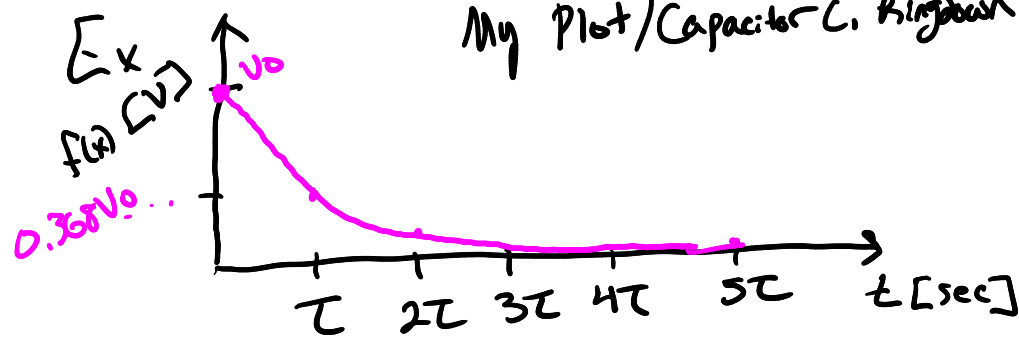


t	$f(x)$
0	V_0
τ	$0.368 V_0$
2τ	$0.135 V_0$
5τ	$0.007 V_0$

* Review

Circuits $\rightarrow R \Rightarrow$ Resistance $[\Omega]$
 $\rightarrow C \Rightarrow$ Capacitance $[F]$
 $\rightarrow L \Rightarrow$ Inductance $[H]$

* Energy Storage Elements

$$C = \frac{\epsilon A}{d}$$

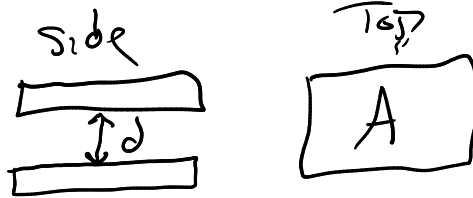

ϵ is dielectric constant / permittivity $\epsilon = \epsilon_r \epsilon_0$ $\epsilon_0 = 8.854 \times 10^{-12}$

$$* Q = CV \Rightarrow i_c = C \frac{dV}{dt}$$

$\frac{Q}{S} = \text{Current!!}$


$$* V(t) = \frac{1}{C} \int_{-\infty}^t i_c(\tau) d\tau = \underbrace{\frac{1}{C} \int_{-\infty}^{t_0} i_c(\tau) d\tau}_{\text{Initial Condition}} + \frac{1}{C} \int_{t_0}^t i_c(\tau) d\tau$$

$$V(t) = V(t_0) + \frac{1}{C} \int_{t_0}^t i_c(\tau) d\tau$$


* Energy Storage in a Capacitor

$$W(t) = \frac{1}{2} C V(t)^2$$

* Series and parallel Capacitors

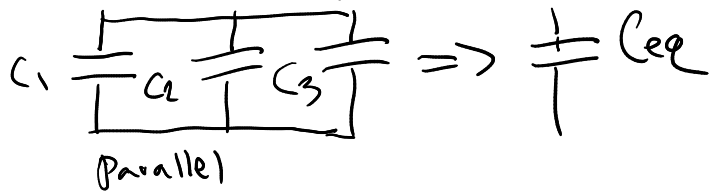
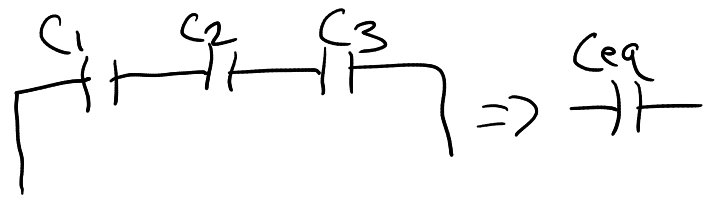
$$C_{eqp} = C_1 + C_2 + C_3 + \dots + C_N$$



Series

$$\frac{1}{C_{eqs}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots + \frac{1}{C_N}$$

* Inductors

$$V(t) = L \frac{di_L}{dt}$$

Where

$$L = \frac{\mu N^2 A}{l}$$

$N = \# \text{ of turns}$
 $\mu = \text{permeability}$

length
 "lower-case l"
 Cursive L

$$\mu = \mu_0 \mu_r \Rightarrow \mu_0 = 4\pi \times 10^{-7}$$

$$i(t) = i(t_0) + \frac{1}{L} \int_{t_0}^t V(\tau) d\tau$$

* Energy Storage in Inductor

$$W(t) = \frac{1}{2} L i(t)^2$$

* Series and parallel Inductors



$$L_{eq} = L_1 + L_2 + L_3 + \dots + L_N$$



Parallel

$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} + \dots + \frac{1}{L_N}$$

* First Order Response


$$V_C(t) = V(\infty) + [V(0) - V(\infty)] e^{-\frac{t}{\tau}}$$

Where $\tau = RC$

$$i_L(t) = i(\infty) + [i(0) - i(\infty)] e^{-\frac{t}{\tau}}$$

Where $\tau = \frac{L}{R}$

* Example

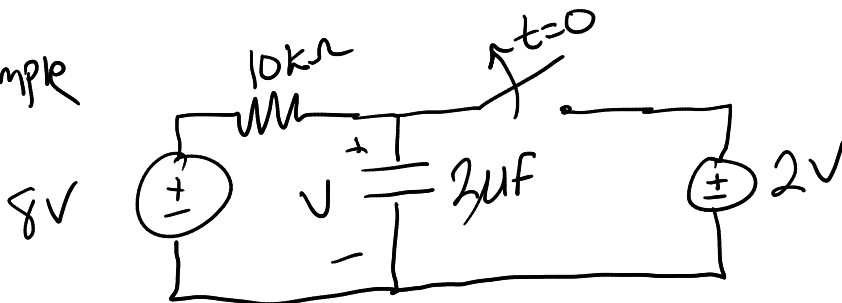


Plot the capacitor voltage as a function of time

$$t < 0^- \quad V(t) = V(\infty) + [V(0) - V(\infty)]e^{-\frac{t}{\tau}}$$



From inspection, $V(0) = 2V$

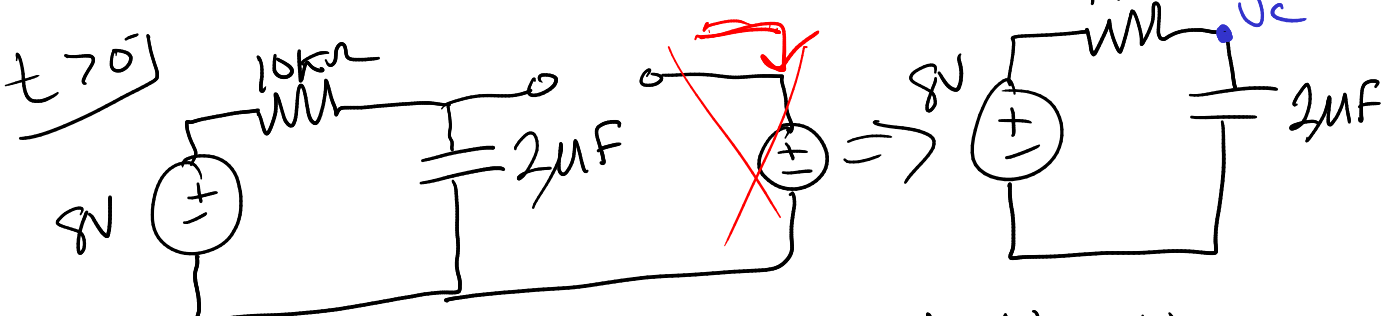

$$\tau = RC = (10 \times 10^3)(2 \times 10^{-6}) = 20 \text{ ms}$$

$$V(\infty) = V_{oc} = V_{th} = 8V$$

$$V(t) = 8 + [2 - 8]e^{-\frac{t}{20 \times 10^{-3}}}$$

$$= 8 - 6e^{-\frac{t}{20 \times 10^{-3}}}$$

$-\frac{t}{20 \times 10^{-3}}$	$t(\text{ms})$	$V(t)$
$-\tau = -20$		2V
0		2V
τ 20		5.793V
2τ 40		7.188V
3τ 60		7.761V
\vdots		
6τ 120		7.985V

