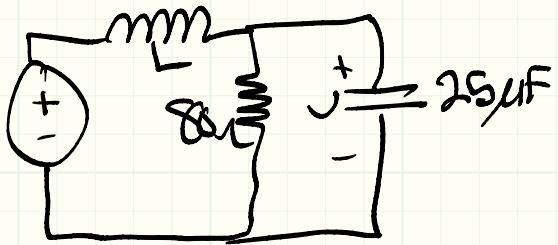


$$L = 1 \text{ H}, V_s = 0 \text{ for } t > 0$$

$$V(0) = 6 \text{ V} \quad \frac{dV(t)}{dt} = -3000 \text{ V/S} \quad V_s$$



Parallel RLC

$$\Rightarrow \alpha = \frac{1}{2RC} \quad \omega_0^2 = \frac{1}{LC}$$

$$\alpha = \frac{1}{2 \times 80 \times 25 \times 10^{-6}} = 250 \text{ rad/sec}$$

$$\omega_0^2 = \frac{1}{LC} = \frac{1}{1 \times 25 \times 10^{-6}} = 40,000 \text{ rad/sec}^2$$

$\alpha^2 > \omega_0^2 \Rightarrow$ overdamped circuit

$$V_n = A_1 e^{S_1 t} + A_2 e^{S_2 t}$$

$$S_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} \quad S_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

$$S_1 = -100$$

$$S_2 = -400$$

$$V(0) = A_1 + A_2 \Rightarrow 6 = A_1 + A_2$$

$$S_1 A_1 + S_2 A_2 = \frac{dV(0)}{dt} \Rightarrow -100A_1 - 400A_2 = -3000$$

$$\text{or } A_1 + 4A_2 = 30$$



$$A_1 = 6 - A_2$$

$$6 - A_2 + 4A_2 = 30$$

$$\Rightarrow 3A_2 = 24 \Rightarrow A_2 = 8$$

$$A_1 = 6 - 8 = -2$$

$$\therefore V_n(t) = -2e^{-100t} + 8e^{-400t} \text{ V}$$

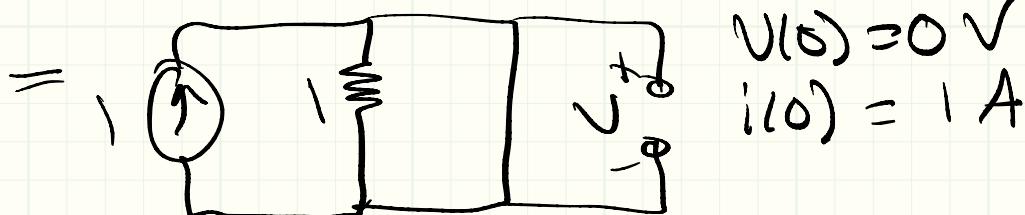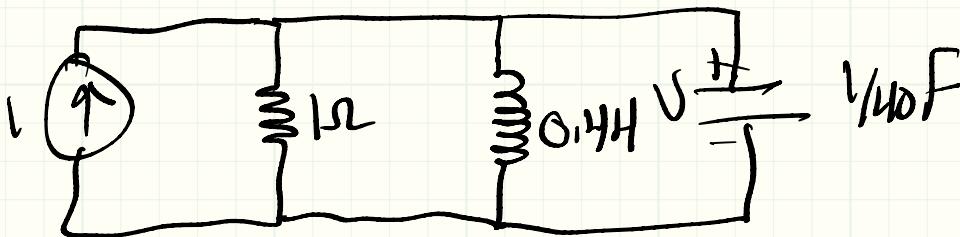for $t < 0$ 

$$V(0) = 0 \text{ V}$$

$$i(0) = 1 \text{ A}$$

for $t > 0$

parallel RLC

$$\alpha = \frac{1}{2RC} = \frac{1}{2(1)(0.4)} = 2.5 \text{ rad/sec}$$

$$\omega_0^2 = \frac{1}{LC} = \frac{1}{0.4 \times 0.4} = 62.5 \text{ rad/sec}^2$$

 $\omega^2 > \omega_0^2 \Rightarrow$ overdamped

$$V_L(t) = A_1 e^{S_1 t} + A_2 e^{S_2 t}$$

$$S_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$$

$$S_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

$$S_1 = -2.7$$

$$S_2 = -37.3$$


$$V(0) = A_1 + A_2 \Rightarrow A_1 + A_2 = 0 \text{ or } A_1 = -A_2$$

$$S_1 A_1 + S_2 A_2 = -\frac{V(0)}{RC} - \frac{i(0)}{C}$$

$$-2.7 A_1 - 37.3 A_2 = -40 \text{ or } A_1 + 13.8 A_2 = 14.8$$

$$\Rightarrow 12.8 A_2 = 14.8 \Rightarrow A_2 = 1.16, A_1 = -1.16$$

$$V_L(t) = -1.16 e^{-2.7t} + 1.16 e^{-37.3t} \quad \checkmark$$

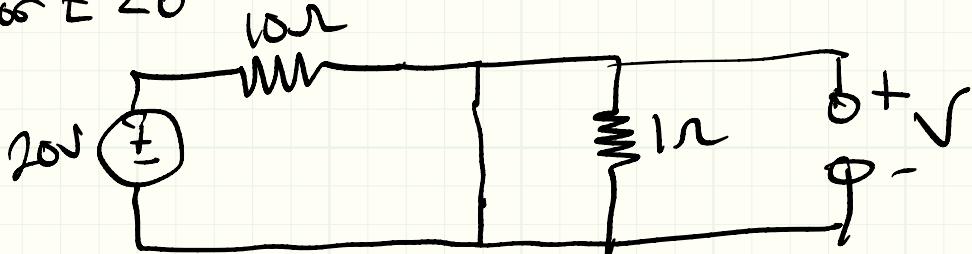For $t < 0$ 

$$V_c(0) = 0 \text{ V} \quad i(0) = \frac{20}{10} = 2 \text{ A}$$

@ $t > 0$

$$\alpha = \frac{1}{2RC} = \frac{1}{2 \times 1 \times \frac{1}{4}} = 2$$

$$\omega_0^2 = \frac{1}{LC} = \frac{1}{1 \times \frac{1}{4}} = 4 \text{ rad/sec}^2$$

$\alpha^2 = \omega_0^2 \therefore$ Critically damped

$$V_L = (A_1 t + A_2) e^{-2t} \quad s.t. \quad S_{1,2} = -\alpha = -2$$

$$\Rightarrow V_L = (A_1 t + A_2) e^{-2t}$$

$$V_L(0) = 0 = A_2 \Rightarrow A_2 = 0$$

$$\frac{V(0)}{R} + i(0) + C \frac{dV(0)}{dt} = 0 \Rightarrow C \frac{dV(0)}{dt} = -i(0) - \frac{V(0)}{R}$$

$$\Rightarrow \frac{1}{4} \frac{dV(0)}{dt} = -2 - 0 \Rightarrow \frac{dV(0)}{dt} = -8$$

finding $\frac{dV}{dt}$ from V_L

$$\frac{dV_L}{dt} = (-2) A_1 t e^{-2t} + e^{-2t} (A_1) - 2 A_2 e^{-2t}$$

$$\frac{dV_L(0)}{dt} = A_1 \Rightarrow A_1 = -8$$

$$V_L = -8t e^{-2t} \quad \checkmark$$

9.5-2 for i_N

4

Solving for current through L

$$\frac{V}{R} + i + C \frac{dV}{dt} = 0 \text{ also } V = L \frac{di}{dt}$$

$$\frac{L}{R} \frac{di}{dt} + i + LC \frac{d^2i}{dt^2} = 0$$

$$\Rightarrow \frac{d^2i}{dt^2} + \frac{1}{RC} \frac{di}{dt} + \frac{1}{LC} i = 0$$

$$i_N = (A_1 t + A_2) e^{-2t}$$

$$i(0) \Rightarrow A_2 = 2$$

$$V(0) = L \frac{di(0)}{dt} \Rightarrow \frac{di(0)}{dt} = 0$$

From Q3

$$\alpha = 2$$

$$\omega_0^2 = 4$$

$$\zeta = -2$$

$$i(0) = 2$$

$$V(0) = 0$$

$$\frac{di}{dt} = -2(A_1 t + A_2) e^{-2t} + e^{-2t} (A_1)$$

$$\frac{di(0)}{dt} = -2A_2 + A_1 \Rightarrow -2(2) + A_1 = 0$$

$$\Rightarrow A_1 = 4$$

$$i_N = (4t + 2) e^{-2t} A$$