
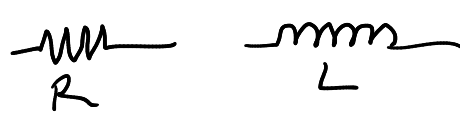


Lecture 2)

Ex:

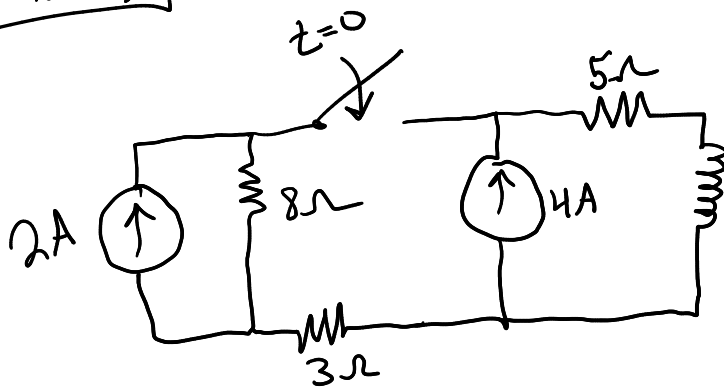

Find $i_L(t)$

$i_L(t)$


$$i_L(0^-) = i_L(0^+) = i_L(0)$$

* We cannot have instantaneous change in current


$$i_L(0) = 4A$$

How do we solve this?

$t < 0$

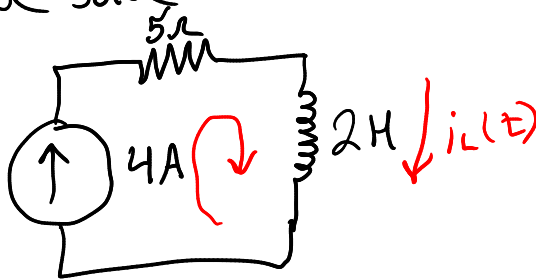


$t > 0^-$

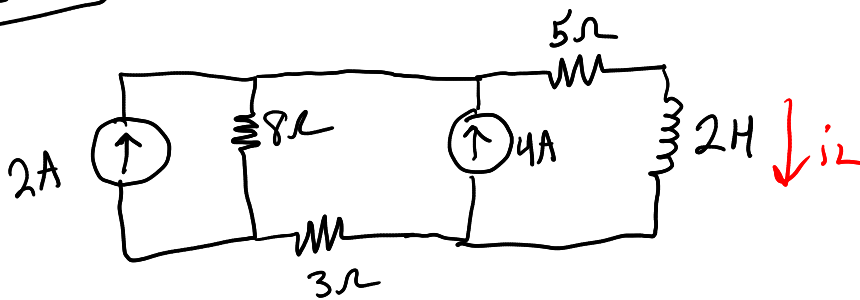


Find $i_L(\infty)$

Use Superposition

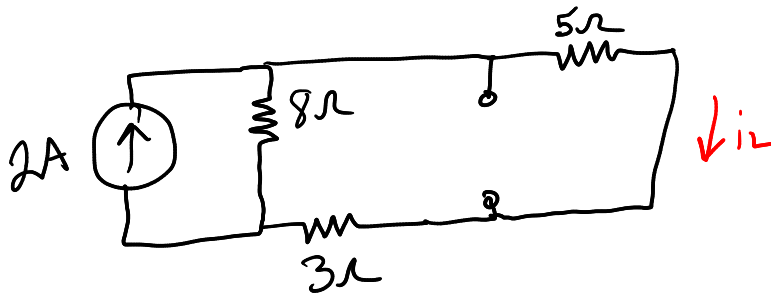
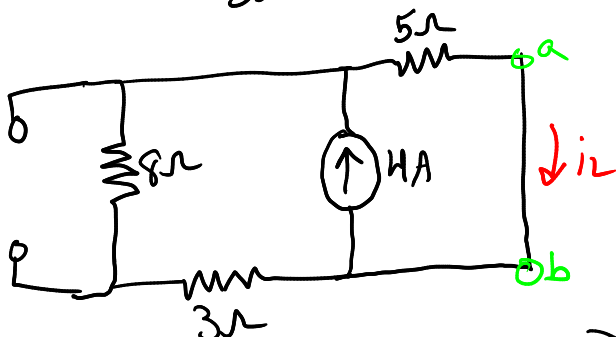
$$i_2(\infty) = \frac{8 \times 2}{5+3+8} = \frac{16}{16} = 1A$$




$$i_4(\infty) = \frac{11 \times 4}{8+3+5} = 2.75A$$

$$i_L(\infty) = i_2(\infty) + i_4(\infty) = 3.75A$$

$$\tau = \frac{L}{R}; L = 2H$$
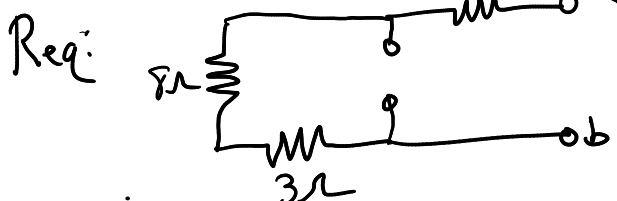
$$i(t) = i(\infty) + [i(0) - i(\infty)] e^{-\frac{t}{\tau}}$$




$$R_{eq} = ?? = 5+8+3 = 16\Omega$$

$$\Rightarrow \tau = \frac{2}{16} = \frac{1}{8}$$

$$i(t) = 3.75 + 0.25 e^{-8t} \text{ A}$$


* Sequential Switching

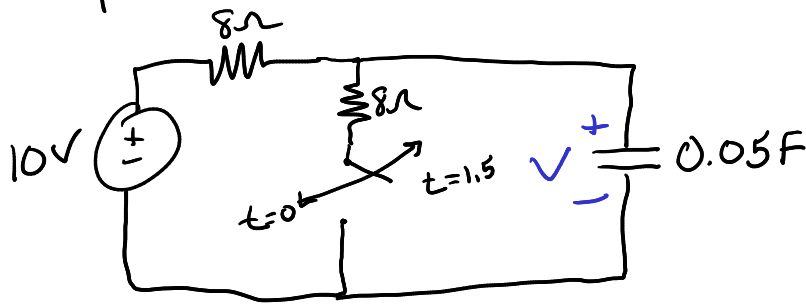

Switch closes
@ $t = 0$


Remains closed till $t = 1.5 \text{ sec}$,
open afterward

for $t < 0$

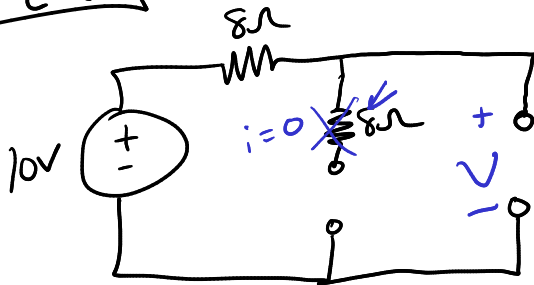


$$V(0) = 10\text{V}$$

for $0 < t < 1.5$

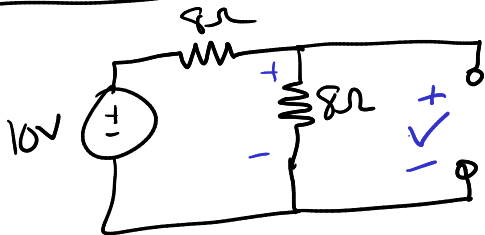

$$V(\infty) = \frac{8}{8+8} \times 10 = 5\text{V}$$
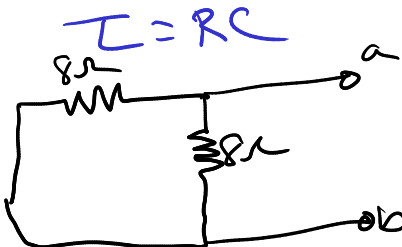
$$V(t) = V(\infty) + [V(0) - V(\infty)] e^{-\frac{t}{\tau}}$$



$$R_{eq} = 8 \parallel 8 = 4\Omega \Rightarrow \tau = 4 \times 0.05 = 0.20 \text{ sec}$$

$$V(t) = 5 + [10 - 5] e^{-\frac{t}{0.20}}$$

$$\Rightarrow 5 + 5 e^{-3t} \checkmark$$

for $0 < t < 1.5 \text{ sec}$

for $t > 1.5$

$$V(1.5) = V(1.5^-) = V(1.5^+)$$

$$V(1.5) = 5 + 5 e^{-5(1.5)} = 5.002\text{V}$$

$$\tau = RC$$

$$\tau = 8(0.05)$$


$$V(\infty) = 10\text{V} \text{ * From earlier}$$

$$\tau = 0.40 \text{ sec}$$

$$V(t) = 10 + [-4.998] e^{-\frac{(t-1.5)}{0.40}} \checkmark$$


* Unit Step
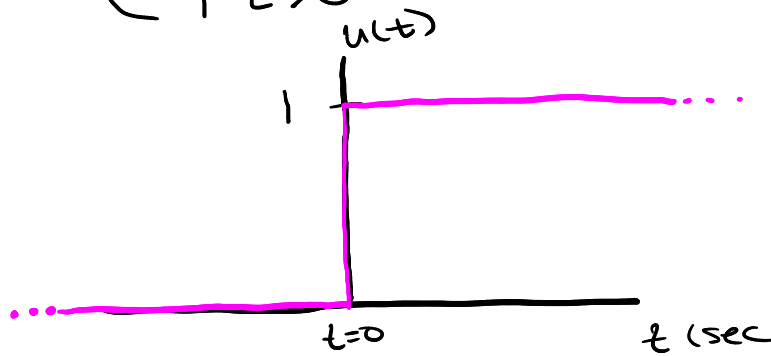
$$u(t) = \begin{cases} 0 & t < 0 \\ 1 & t > 0 \end{cases}$$




* Time Delay
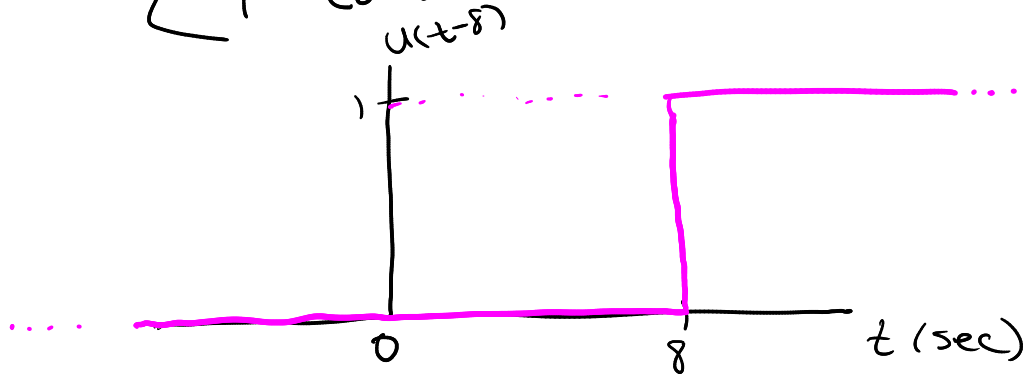
$$u(t-8) = \begin{cases} 0 & (t-8) < 0 \\ 1 & (t-8) > 0 \end{cases} = \begin{cases} 0 & t < 8 \\ 1 & t > 8 \end{cases}$$





* Time Reversal
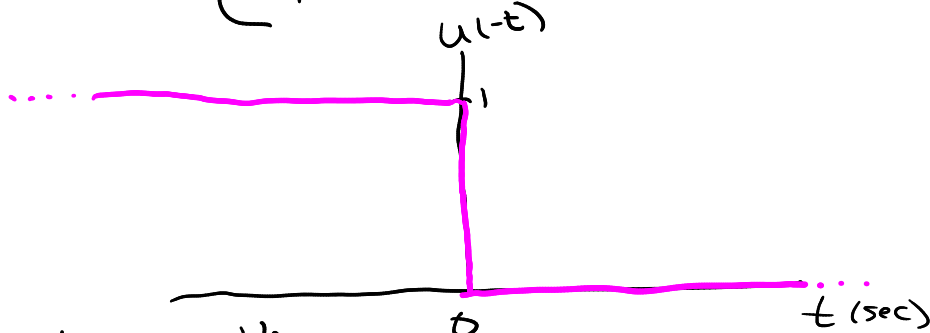
$$u(-t) = \begin{cases} 0 & (-t) < 0 \\ 1 & (-t) > 0 \end{cases} = \begin{cases} 0 & t > 0 \\ 1 & t < 0 \end{cases}$$




* $V(t) = 3u(-t) - 7u(t)$ Volts V_1

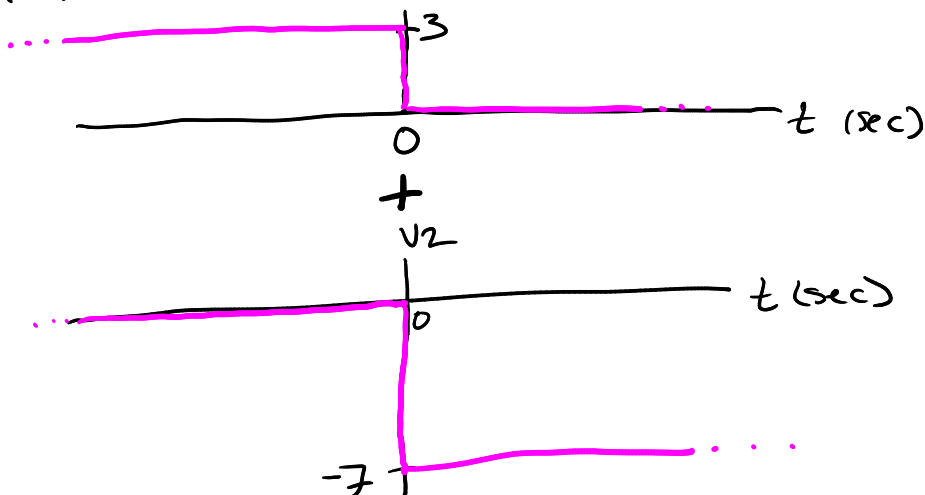

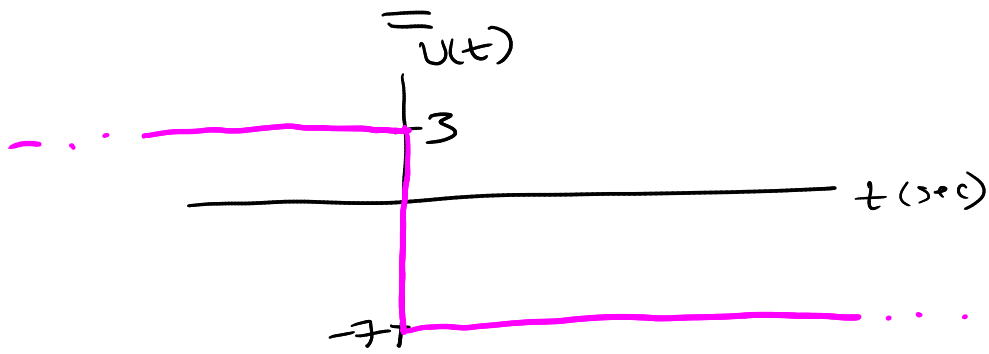


* Pulse

$$V(t) = 2 [u(t+3) - u(t-4)]$$

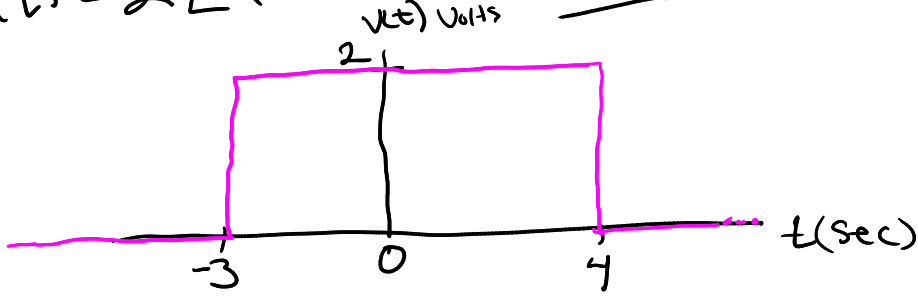

* Example

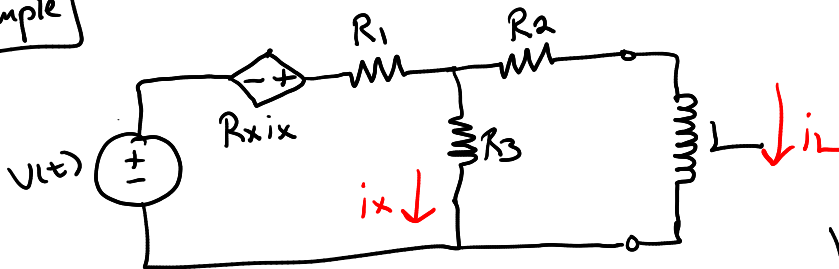

Given

$$R_1 = 8\Omega, R_2 = 1.6\Omega$$

$$R_3 = 4\Omega, R_x = 2\Omega$$

$$L = 3H$$

$$V(t) = -9u(-t) + 6u(t) \checkmark$$


a) Find $i_L(t)$ over $-\infty < t < \infty$

b) Plot $i_L(t)$ over $-7 < t < 5$


* Take a good look at $V(t)$

$$i_L(t) = i(\infty) + [i(0) - i(\infty)] e^{-\frac{t}{\tau}}$$

$$\tau = \frac{L}{R_{eq}}$$

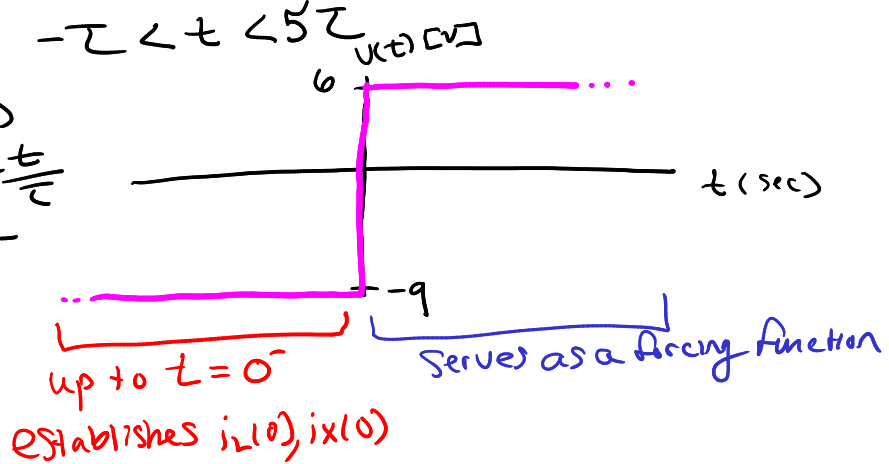

$t < 0$ assume DCSS

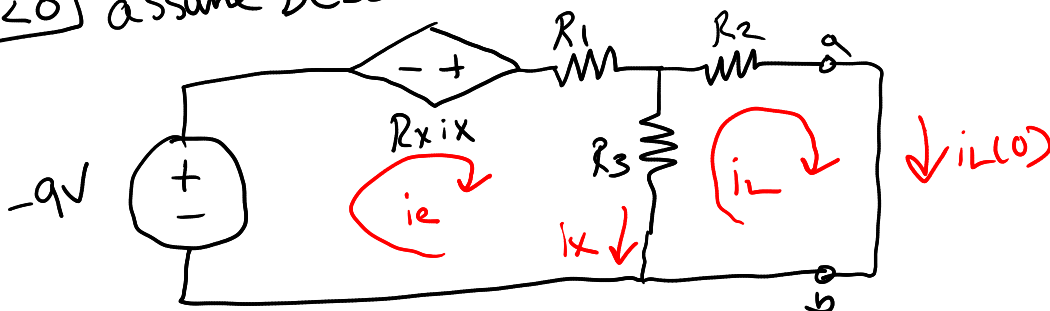

Note $ix(0) = ie - i_L$

Using mesh analysis


$$ie) \quad 9 - R_x i_x + R_1 i_e + R_3 (i_e - i_L)$$

$$\Rightarrow -R_x(i_e - i_L) + R_1(i_e) + R_3(i_e - i_L) = -9 \quad (1)$$

$$\xrightarrow{i_L} R_3(i_L - i_e) + R_2 i_L = 0 \quad (2)$$

* Solving these equations yields $i_L(0) = -0.75A$, $i_x(0) = -0.3A$

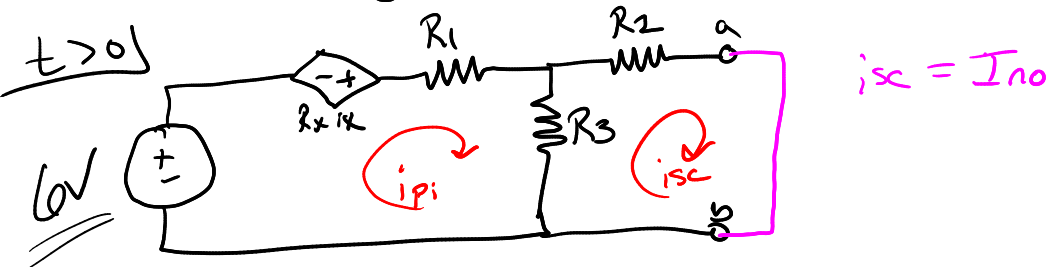* Find i_{sc} and R_{eq} seen at port a,b for $t > 0$



Mesh yields $i_{sc} = 0.5A$


Need R_{eq} , we have 2 approaches

* can use $R_{eq} = \frac{V_{oc}}{I_{sc}} = \frac{V_{th}}{I_{no}}$

* Can turn off independent sources then apply

either $\oplus 1V$ or $\uparrow 1A$ to a,b

I will seek V_{oc}

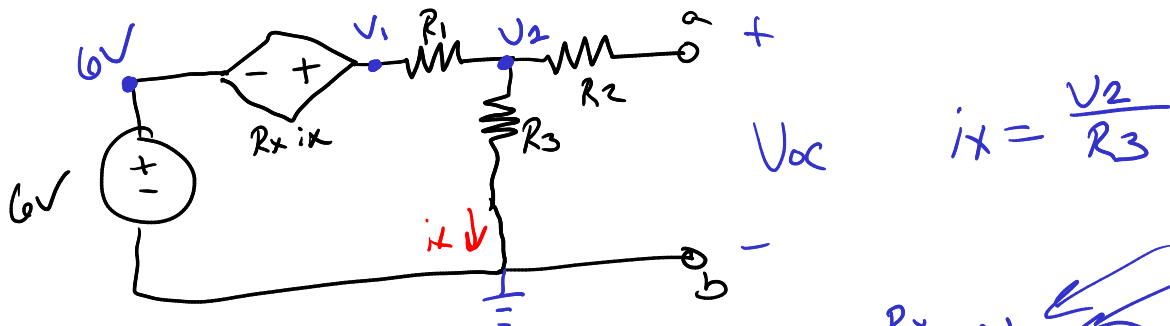

Using Nodal $V_1 - 6 = R_x i_x \Rightarrow V_1 - 6 = \frac{R_x}{R_3} V_2$

$$\xrightarrow{V_2} \frac{V_2 - V_1}{R_1} + \frac{V_2 - 0}{R_3} = 0 \Rightarrow \left(-\frac{1}{R_1}\right)V_1 + \left(\frac{1}{R_1} + \frac{1}{R_3}\right)V_2 = 0 \quad (1)$$

$$(1)V_1 + \left(-\frac{R_x}{R_3}\right)V_2 = 6 \quad (2)$$

Solving yields

$$V_1 = 7.2V \quad V_2 = 2.4V = V_{oc}$$

$$R_{eq} = \frac{2.4V}{0.5A} = 4.8\Omega$$

$$i_L(t) = \begin{cases} -0.75 \text{ A} & t < 0 \\ 0.5 - 1.25 e^{-\frac{t}{0.025}} & t > 0 \end{cases}$$

