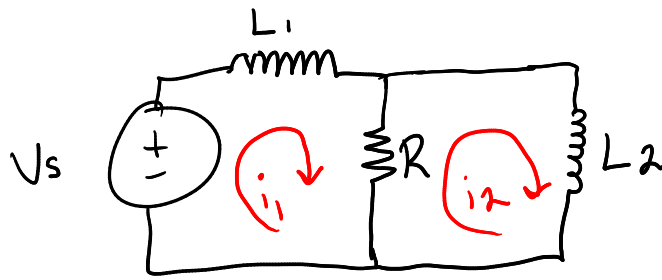


Lecture 4

Continuing Second Order Circuits

Method 2: Operator Method



Given

$$R = 1 \Omega$$
$$L_1 = 1 H$$
$$L_2 = 2 H$$
$$V_L = L \frac{di}{dt}$$

$$i_1) -V_s + V_{L1} + R(i_1 - i_2) = 0$$
$$\Rightarrow L_1 \frac{di_1}{dt} + R(i_1 - i_2) = V_s$$

$$i_2) R(i_2 - i_1) + L_2 \frac{di_2}{dt} = 0$$

Substitute Values

$$\frac{di_1}{dt} + i_1 - i_2 = V_s \quad (1) \leftarrow * \text{ differential } \Rightarrow \frac{d}{dt} = s$$

$$i_2 - i_1 + 2 \frac{di_2}{dt} = 0 \quad (2)$$

$$\Rightarrow s i_1 + i_1 - i_2 = V_s \Rightarrow (s+1) i_1 - i_2 = V_s$$

$$\Rightarrow i_2 - i_1 + 2s i_2 = 0 \Rightarrow -i_1 + (2s+1) i_2 = 0$$

* Cramer's Rule for i_2

$$\begin{vmatrix} s+1 & V_s \\ -1 & 0 \end{vmatrix}$$

For i_1

$$\begin{vmatrix} V_s & -1 \\ 0 & 2s+1 \end{vmatrix}$$

$$\begin{vmatrix} a & b \\ c & d \end{vmatrix} = ad - bc$$

$$\frac{\begin{vmatrix} s+1 & V_s \\ -1 & 0 \end{vmatrix}}{\begin{vmatrix} s+1 & -1 \\ -1 & 2s+1 \end{vmatrix}} = \frac{0 - (-V_s)}{[2s^2 + 3s + 1] - (1)}$$

$$\Rightarrow \frac{V_s}{2s^2 + 3s} = i_2 \quad \text{or} \quad V_s = i_2 (2s^2 + 3s)$$

* Sub back in $\frac{d}{dt}$

Divide by 2

$$2 \frac{d^2 i_2}{dt^2} + 3 \frac{di_2}{dt} = V_s$$

$$\Rightarrow \frac{d^2 i_2}{dt^2} + \frac{3}{2} \frac{di_2}{dt} = \frac{1}{2} V_s$$

$$2\alpha = \frac{3}{2} \quad \omega_0^2 = 0$$


$$\alpha = \frac{3}{4}$$

$$\omega_0 = 0$$

* Steps for the operator method

- 1) Identify the variable for which the solution is desired
- 2) Write 2 differential equations in terms of x_1 and x_2
- 3) Use the operator $s = \frac{d}{dt}$ and $\frac{1}{s} = \int dt$ to obtain 2 algebraic equations
- 4) Use Cramer's Rule to solve for desired variable
- 5) Rearrange equation and convert back to derivative form

* Example

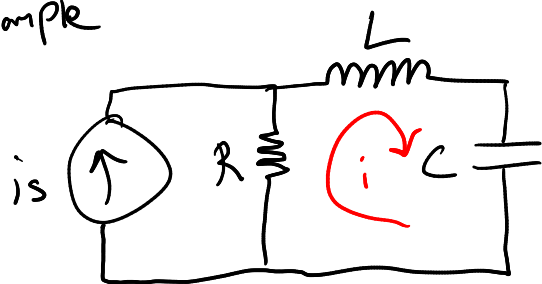

Given

$$R = 1 \Omega$$

$$L = 2 H$$

$$C = 0.5 F$$

Find the 2nd order diff. eq. using the direct method in terms of i

Mesh eq.

$$R(i - i_s) + L \frac{di}{dt} + V_c = 0$$

$$\Rightarrow i - i_s + 2 \frac{di}{dt} + V_c = 0$$

$$\Rightarrow V_c = -i + i_s - 2 \frac{di}{dt}$$

$$\frac{dV_c}{dt} = -\frac{di}{dt} + \frac{di_s}{dt} - 2 \frac{d^2 i}{dt^2}$$

Remember

$$i_c = C \frac{dV_c}{dt}$$

plug in

$$i = -\frac{1}{2} \frac{di}{dt} + \frac{1}{2} \frac{dis}{dt} - \frac{d^2i}{dt^2}$$

* Multiply $\frac{dV}{dt}$ by $C = \frac{1}{2} = 0.5$

Rearrange

$$\frac{d^2i}{dt^2} + 0.5 \frac{di}{dt} + i = 0.5 \frac{dis}{dt} \text{ Amp}$$


$$2\alpha = \frac{1}{2}$$

$$\omega_0^2 = 1$$

$$\therefore \alpha = 0.25$$

$$\omega_0 = 1 \frac{\text{rad}}{\text{s}}$$

* Example

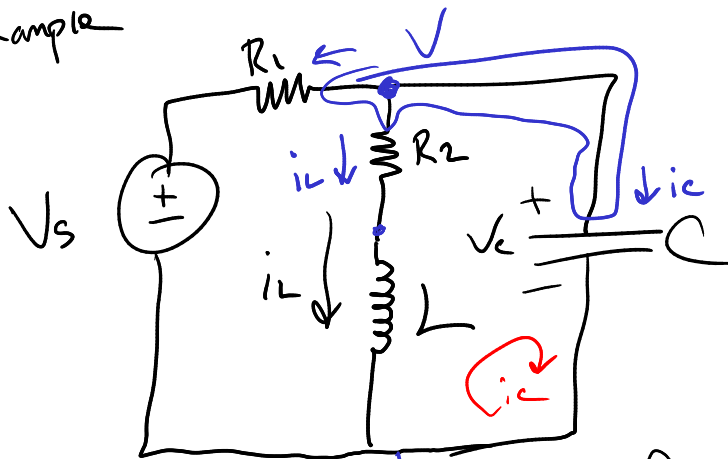

Given

$$R_1 = 1 \text{ k}\Omega$$

$$R_2 = 1 \Omega$$

$$L = 1 \text{ mH}$$

$$C = 1 \text{ mF}$$

Find the differential equation for the voltage V_c using the operator method

$$x_1 = i_L$$

$$x_2 = V_c$$

At Node V

$$\frac{1}{R_1} (V - V_s) + i_L + C \frac{dV}{dt} = 0 \leftarrow$$

Current through inductor

$$V_c = i_L R_2 + L \frac{di_L}{dt} \Rightarrow i_L R_2 + L \frac{di_L}{dt} - V_c = 0$$

$$\frac{d}{dt} \rightarrow s$$

$$(1) i_L + \left(\frac{1}{R_1} + sC \right) V = \frac{V_s}{R_1} \quad (1) \quad \times R_1$$

Replace $\frac{d}{dt} \rightarrow s$

$$i_L R_2 + sL i_L - V = 0$$

$$(R_2 + sL) i_L + (-1) V = 0 \quad (2)$$

$$R_1 i_L + (1 + sR_1 C) V = V_s \quad (3)$$

* Cramer's Rule

$$\frac{\begin{vmatrix} R_1 & V_s \\ R_2 + sL & 0 \end{vmatrix}}{\begin{vmatrix} R_1 & 1 + sR_1 C \\ R_2 + sL & -1 \end{vmatrix}} = \frac{0 - (R_2 + sL)V_s}{-R_1 - (1 + sR_1 C)(R_2 + sL)}$$

$$= \frac{-(R_2 + sL)V_s}{-R_1 - [R_2 + sL + sR_1 R_2 C + s^2 R_1 L C]}$$

$$= \frac{-(R_2 + sL)V_s}{[-R_1 L C]s^2 - [L + R_1 R_2 C]s - [R_1 + R_2]}$$

Plug in values

$$\Rightarrow \frac{-(1 + 10^{-3}s)V_s}{-10^{-3}s^2 - [10^{-3} + 1]s - [10^3 + 1]}$$

$$10^{-3} + 10^3 \times 10^{-3}$$

Divide by 10^{-3}
and factor out -1
from denominator

$$= \frac{(s + 1000)V_s}{s^2 + 1001s + 1001 \times 10^3} = V_c$$

* Rearrange and convert back

$$V_c (s^2 + 1001s + 1001 \times 10^3) = (s + 1000)V_s$$

$$\Rightarrow \left[\frac{d^2 V_c}{dt^2} + 1001 \frac{dV_c}{dt} + 1001 \times 10^3 V_c = \frac{dV_s}{dt} + 1000 V_s \right] \quad V_c(t) \quad V_s(t)$$

* Solution of 2nd order differential equation

Equation is of the form

$$a_2 \frac{d^2x}{dt^2} + a_1 \frac{dx}{dt} + a_0 = f(t)$$

Where a_2, a_1, a_0 are known constants
and $f(t)$ is the forcing function.

* The complete response $x(t)$ is given by

$$x(t) = \underbrace{x_n}_{\text{Natural Response}} + \underbrace{x_f}_{\text{Forced Response}}$$

The natural response \longrightarrow when $f(t) = 0$

The forced response \longrightarrow when $f(t) \neq 0$

* The natural response will satisfy the equation

$$a_2 \frac{d^2x_n}{dt^2} + a_1 \frac{dx_n}{dt} + a_0 x_n = 0$$

Where $x_n = Ae^{st}$

$$\frac{dx_n}{dt} = sAe^{st} \Rightarrow \frac{d^2x_n}{dt^2} = s^2Ae^{st}$$

$$a_2 s^2 Ae^{st} + a_1 s Ae^{st} + a_0 Ae^{st} = 0$$

Add x_n back and factor

$$\Rightarrow (a_2 s^2 + a_1 s + a_0) x_n = 0$$

* Since $x_n \neq 0$ is a trivial solution, we require

$$\underbrace{a_2 s^2 + a_1 s + a_0}_{\text{Characteristic Equation}} = 0 \quad s^n = \frac{d^n}{dt^n} \text{ holds}$$


$$s_1 = \frac{-a_1 + \sqrt{a_1^2 - 4a_2a_0}}{2a_2}$$

$$s_2 = \frac{-a_1 - \sqrt{a_1^2 - 4a_2a_0}}{2a_2}$$

* When there are two roots,

$$X_n = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

* Example

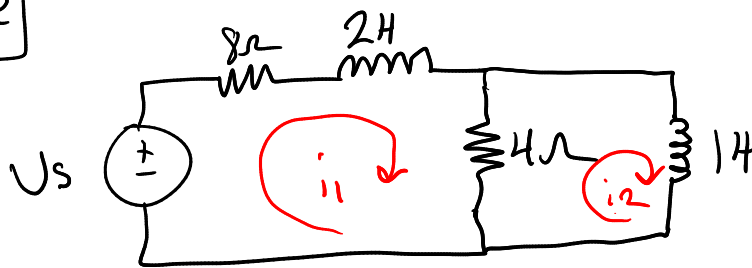

Find the natural response of the current i_2

Mesh i_1

$$-V_s + 8i_1 + 2 \frac{di_1}{dt} + 4(i_1 - i_2) = 0$$

$$\Rightarrow 12i_1 + 2 \frac{di_1}{dt} - 4i_2 = V_s \quad (1)$$

Mesh i_2

$$4(i_2 - i_1) + \frac{di_2}{dt} = 0$$

$$\Rightarrow -4i_1 + 4i_2 + \frac{di_2}{dt} = 0 \quad (2)$$

Use $s = \frac{d}{dt}$

$$(12 + 2s)i_1 - 4i_2 = V_s$$

$$-4i_1 + (4 + s)i_2 = 0$$

$$i_2 = \frac{\begin{vmatrix} 12+2s & V_s \\ -4 & 0 \end{vmatrix}}{\begin{vmatrix} 12+2s & -4 \\ -4 & 4+s \end{vmatrix}} = \frac{0 - (-4V_s)}{48 + 20s + 2s^2 - 16}$$

$$\Rightarrow \frac{4V_s}{2s^2 + 20s + 32} = \frac{2V_s}{s^2 + 10s + 16} = i_2$$

Divide by 2

$$\Rightarrow (s^2 + 10s + 16)i_2 = 2V_s$$

Characteristic Equation

Roots are
 $s_1 = -2$
 $s_2 = -8$

We will find A_1 and A_2 next time

$$X_n = A_1 e^{-2t} + A_2 e^{-8t}$$