
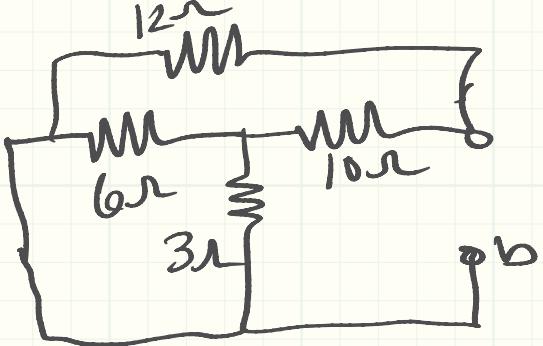


Req


$$\begin{aligned}
 R_{\text{eq}} &= [3/(6+10)] || 12 = [2+10] || 12 \\
 &= 6\Omega \\
 T &= R_{\text{eq}} C = 6 * \frac{1}{24} = \frac{1}{4} \text{ sec}
 \end{aligned}$$

$$\Rightarrow V(t) = 12 + [0 - 12] e^{-\frac{4t}{6}} V$$

$V(t) = 12 - 12e^{-\frac{4t}{6}} V$

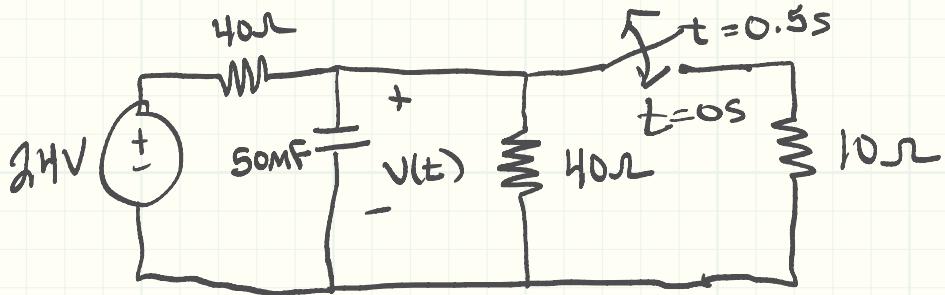


@  $t < 0$

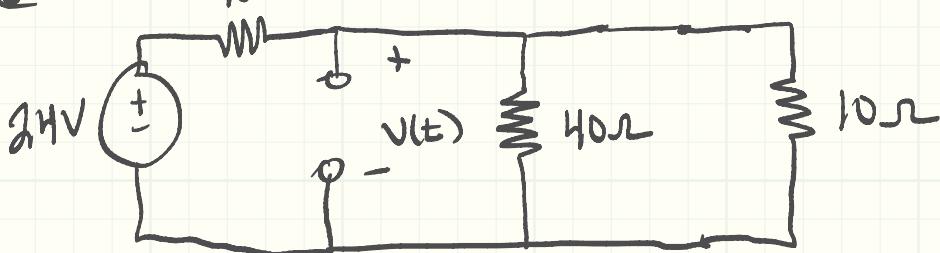


$$40 \parallel 10 = 8\Omega$$

$$V(0) = \frac{8}{40+8} * 24 = 4V$$

@  $t > 0$  and  $t < 0.5s$

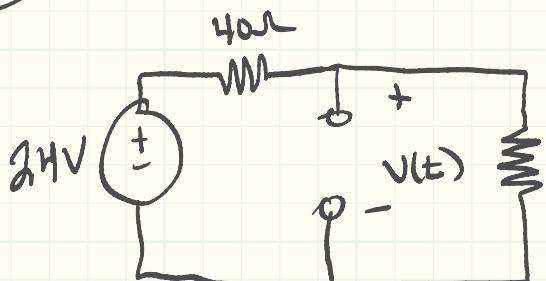
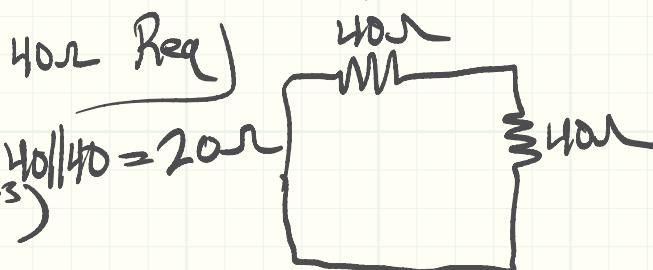
$$V(\infty) = \frac{40}{40+40} * 24 = 12V$$



$$\tau = R_{eq} C = 20(50 \times 10^{-3})$$

$$\tau = 1$$


$$V(t) = V(\infty) + [V(0) - V(\infty)] e^{-\frac{t}{\tau}}$$

$$V(t) = 12 + [4 - 12] e^{-t}$$

$$V(t) = 12 - 8e^{-t}$$


@  $t > 0.5$

$$V(0.5) = 12 - 8e^{-0.5} = 7.148V$$

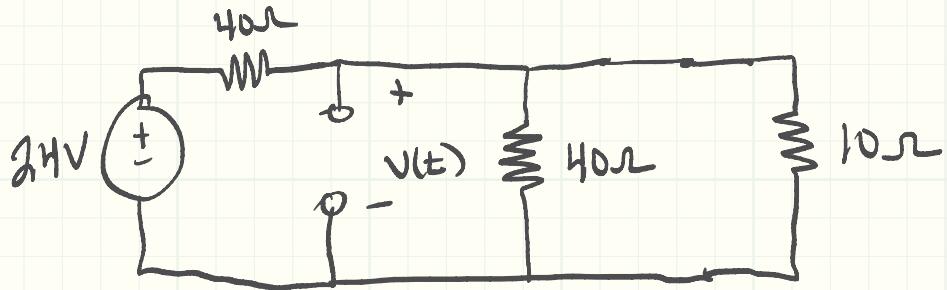

$$V(\infty) = 4V \text{ from earlier}$$

Req

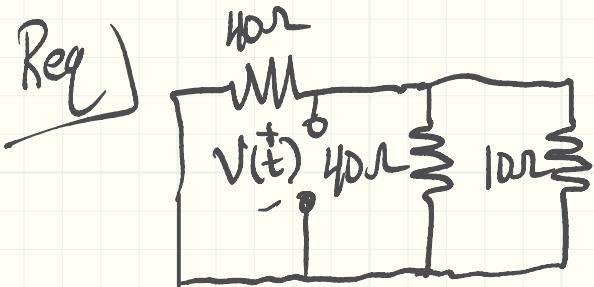

$$R_{\text{eq}} = 4\Omega \parallel 4\Omega \parallel 10\Omega$$

$$R_{\text{eq}} = 6.67\Omega$$

$$\tau = 0.334 \text{ sec}$$

$$-3(t-0.5)$$

$$V(t) = V(\infty) + [V(0.5) - V(\infty)] e^{-3(t-0.5)}$$

$$V(t) = 4 + [7.148 - 4] e^{-3(t-0.5)}$$


$$V(t) = 4 + 3.148 e^{-3(t-0.5)}$$

$V(t)$

$$4V \quad t < 0$$

$$12 - 8e^{-t} \quad 0 \leq t \leq 0.5$$
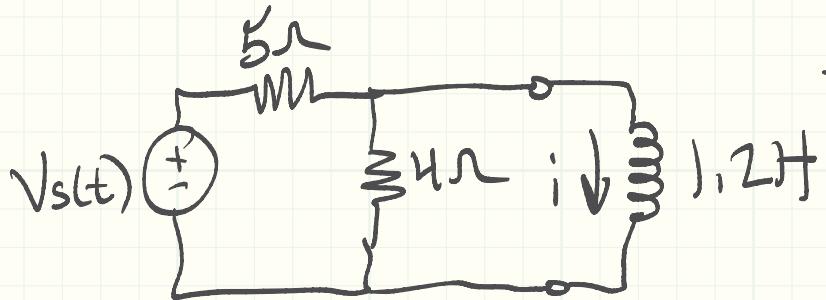
$$4 + 3.148 e^{-3(t-0.5)} \quad t \geq 0.5$$




Given

$$V_s(t) = -7 + 13u(t)$$

for  $t < 0$


$$V_s(t) = -7$$

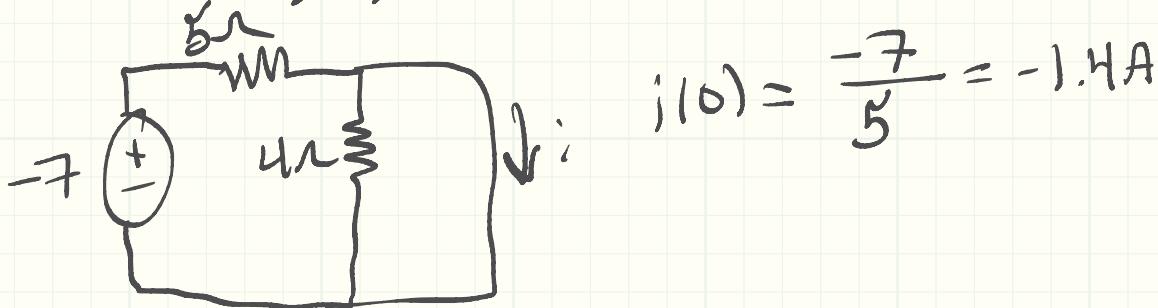


$$i(0) = \frac{-7}{5} = -1.4A$$

for  $t > 0$

$$V_s(t) = 6V$$

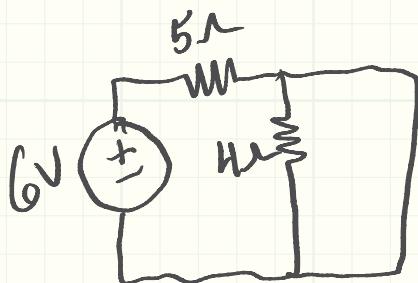

$$i(\infty) = \frac{6}{5} = 1.2A$$

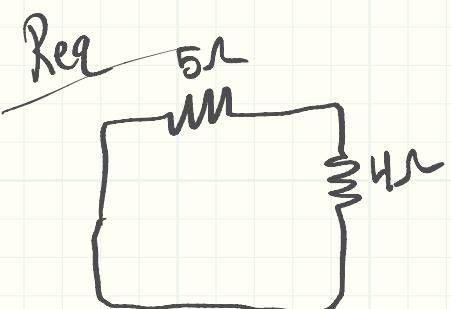


$$5 \parallel 4 = 2.22\Omega$$

$$\tau = \frac{L}{R} = \frac{1.2}{2.22} = 0.54 \text{ sec}$$


$$i_L = i(\infty) + [i(0) - i(\infty)] e^{-\frac{t}{\tau}} A$$

$$i_L = 1.2 - 2.6 e^{-1.85t} A$$

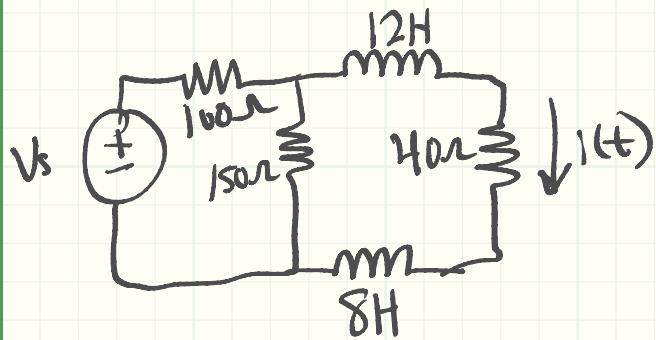

Given

$$V_s(t) = 25u(t) - 10V$$

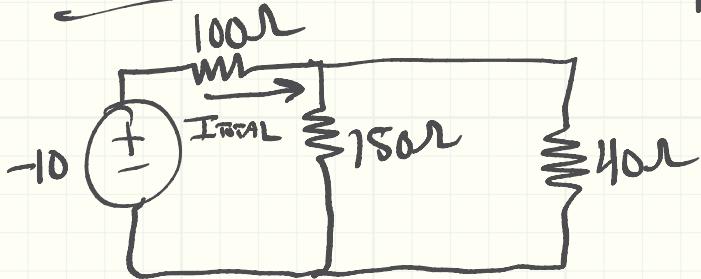 $\text{@ } t < 0$ 

$$i_{\text{TOTAL}} = \frac{-10}{40 \parallel 150 + 100} = \frac{-10}{131.58}$$

$$i_{\text{TOTAL}} = -76mA$$

$$i(0) = \frac{150 \times -76 \times 10^{-3}}{150 + 40}$$

$$i(0) = -60mA$$

 $\text{@ } t > 0$ 




$$\text{Now } V_s = 15V$$

$$i_{\text{TOTAL}} = \frac{15}{131.58} = 114mA$$

$$i(\infty) = \frac{150 + 114 \times 10^{-3}}{150 + 40} = 90mA$$

$$\text{Req) } L = 12 + 8 = 20H$$

$$100 \parallel 150 = 60\Omega$$

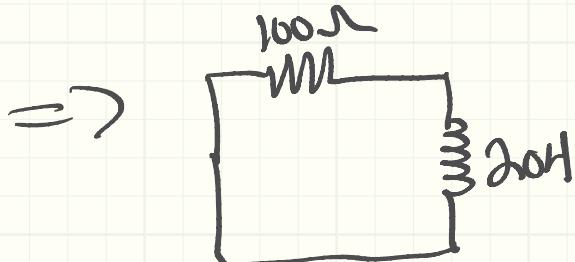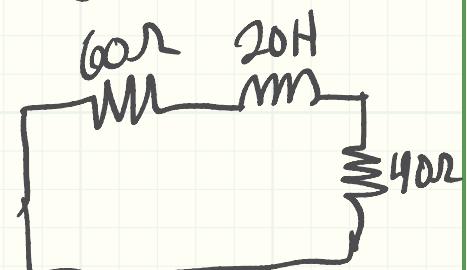
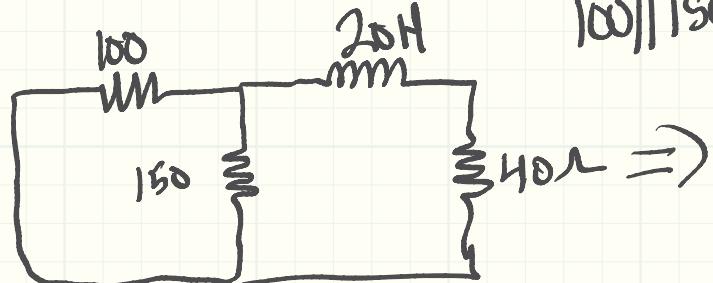


$$\text{Req} = 100\Omega$$

$$\tau = \frac{L}{R} = \frac{20}{100} = \frac{1}{5}$$

$$i(t) = i(\infty) + [i(0) - i(\infty)] e^{-\frac{t}{\tau}}$$
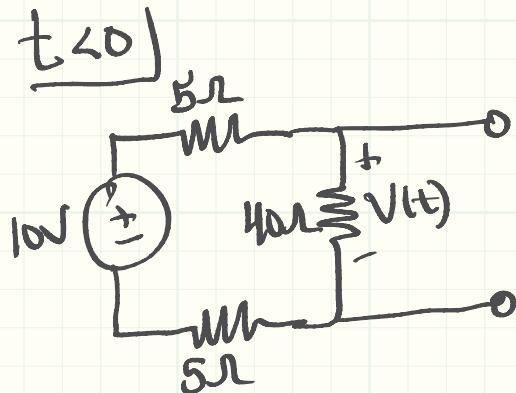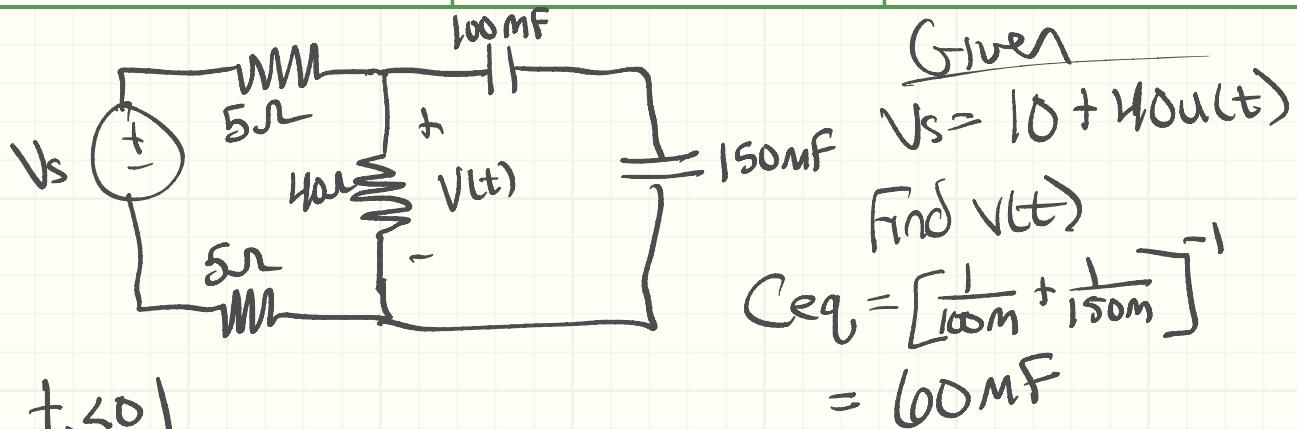
$$i(t) = 90 - 150 e^{-\frac{t}{5}} \text{ mA}$$




$$V(0) = \frac{40}{40+5+5} \times 10 = 8V$$

$@ t > 0$

$$V_s = 50V$$

$$V(\infty) = \frac{40}{40+5+5} \times 50 = 40V$$

Req

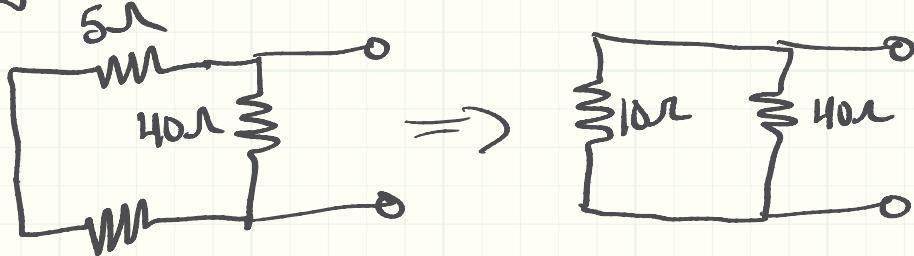

$$R_{eq} = 10 || 40 = 8\Omega$$


$$T = R_{eq} C_{eq} = 8 * 60 * 10^{-3} = 0.48 \text{ sec}$$

$$V(t) = V(\infty) + [V(0) - V(\infty)] e^{-2.083t}$$

$$V(t) = 40 - 32 e^{-2.083t} \quad V$$

# Question 9

14

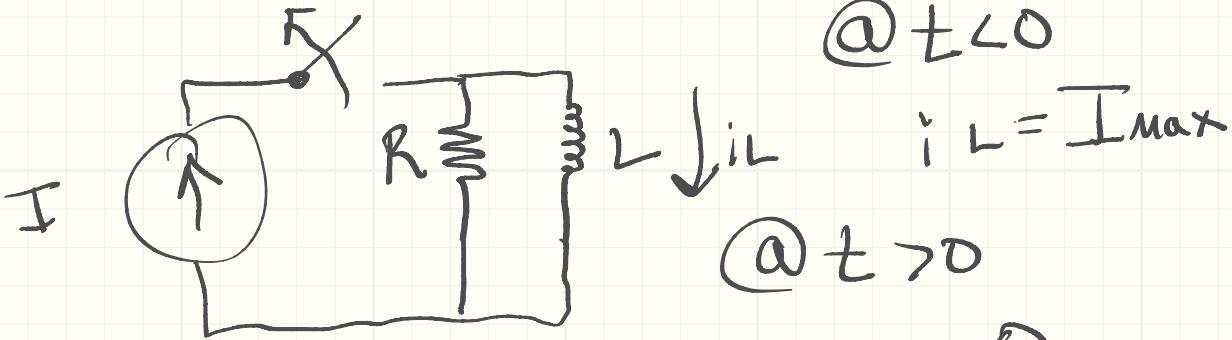

$$i_L(t) = i_L(\infty) + [i(0) - i(\infty)] e^{-\frac{t}{\tau}}$$

$$i_L(t) = 0 + [I_{\max} - 0] e^{-\frac{t}{\tau}}$$

$$\Rightarrow i_L(t) = I_{\max} e^{-\frac{t}{\tau}}$$

$$\Rightarrow i_L(\infty) = I_{\max} e^{-1} = 0.3678 I_{\max}$$