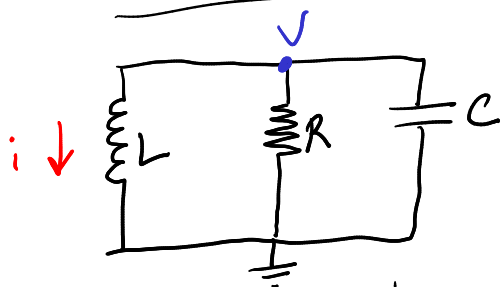


Lecture 5

Natural Response of the Unforced Parallel RLC Circuit



* Circuit will have a second order differential equation

$$\frac{d^2}{dt^2} x(t) + 2\alpha \frac{d}{dt} x(t) + \omega_0^2 x(t) = f(t)$$

No Source

* We will choose the output to be $V(t)$

$$\frac{d^2}{dt^2} V(t) + 2\alpha \frac{d}{dt} V(t) + \omega_0^2 V(t) = 0$$

KCL at V

$$i + i_R + i_C = 0$$

$$\frac{1}{L} \int_0^t V d\tau + \underbrace{i(0)}_{\text{constant}} + \frac{V}{R} + C \frac{dV}{dt} = 0$$

Taking the derivative and rearrange

$$C \frac{d^2 V}{dt^2} + \frac{1}{R} \frac{dV}{dt} + \frac{1}{L} V = 0$$

* Divide by C

$$\frac{d^2 V}{dt^2} + \frac{1}{RC} \frac{dV}{dt} + \frac{1}{LC} V = 0$$

$$\frac{d}{dt} \rightarrow s$$

$$\Rightarrow \left(s^2 + \frac{1}{RC} s + \frac{1}{LC} \right) V = 0$$

Characteristic Equation \Leftrightarrow C.E.

$$2\alpha = \frac{1}{RC}$$

$$\omega_0^2 = \frac{1}{LC}$$

$$\therefore \alpha = \frac{1}{2RC}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

* The two roots of the C.E. are

$$s_1 = -\frac{1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}} \quad \text{and} \quad s_2 = -\frac{1}{2RC} - \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}$$

* When $s_1 \neq s_2$, the solution is

$$V_n = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

* The roots can be written as

$$S_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} \quad \text{and} \quad S_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

* We define the damped resonant frequency as

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2}$$

$\frac{\partial}{\partial t}$ partial

* The roots of the C.E. assume possible conditions:

$\frac{d}{dt}$ time derivative

1) $\alpha^2 > \omega_0^2$ \rightarrow Two real, distinct roots
overdamped

2) $\alpha^2 = \omega_0^2$ \rightarrow Two real, equal roots
critically damped

3) $\alpha^2 < \omega_0^2$ \rightarrow Two complex roots
underdamped

* Considering an overdamped RLC circuit at $t=0$

$$\Rightarrow V_n = A_1 e^{S_1 t} + A_2 e^{S_2 t}$$

$$\boxed{V(0) = A_1 + A_2}$$

We need another equation to solve for A_1 and A_2
Let's solve for the derivative

KCL from earlier

$$\frac{1}{L} \int_0^t v(\tau) d\tau + i(0) + \frac{v}{R} + C \frac{dv}{dt} \leftarrow t=0$$

$$A_1 e^{S_1 t} + A_2 e^{S_2 t}$$

$$S_1 A_1 e^{S_1 t} + S_2 A_2 e^{S_2 t}$$

$$\Rightarrow i(0) + \frac{V(0)}{R} + C \frac{dV(0)}{dt} = 0$$


$$\Rightarrow \frac{dV(0)}{dt} = -\frac{V(0)}{RC} - \frac{i(0)}{C}$$

* Also

$$\frac{dV(0)}{dt} = S_1 A_1 + S_2 A_2$$

$$\Rightarrow \boxed{S_1 A_1 + S_2 A_2 = -\frac{V(0)}{RC} - \frac{i(0)}{C}}$$

* Example

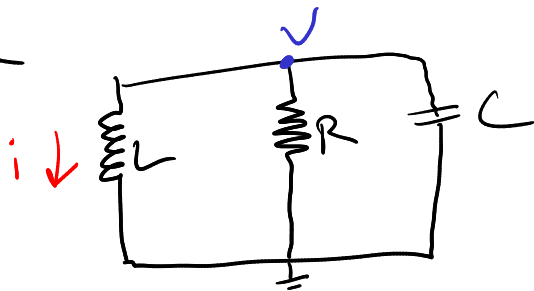

Given

$$R = \frac{2}{3} \Omega, L = 1 \text{ H}$$

$$C = \frac{1}{2} \text{ F}, V(0) = 10 \text{ V}, i(0) = 2 \text{ A}$$

Find the natural response of $V(t)$

$$\text{C.E.} = S^2 + \frac{1}{RC} S + \frac{1}{LC} = 0$$

$$\text{or } s^2 + 3s + 2 = 0 \Rightarrow (s+1)(s+2) = 0$$

$$s_1 = -1 \quad s_2 = -2 \quad \alpha = \frac{1}{2RC} \quad \text{and } \omega_0^2 = \frac{1}{LC}$$

Circuit is overdamped!!!

$$\alpha = \frac{3}{2} \quad \omega_0^2 = 2$$

$$\alpha^2 = \frac{9}{4}$$

$$V_n = A_1 e^{-t} + A_2 e^{-2t}$$

* To Find A_1 and A_2

$$V_n(0) = A_1 + A_2 \Rightarrow A_1 + A_2 = 10$$

$$s_1 A_1 + s_2 A_2 = \frac{-V(0)}{RC} - \frac{i(0)}{C}$$

$$\Rightarrow -A_1 - 2A_2 = \frac{-10}{1/3} - \frac{2}{1/2}$$

$$\Rightarrow -A_1 - 2A_2 = -34$$

$$-10 + A_2 - 2A_2 = -34$$

$$-A_2 = -24 \Rightarrow A_2 = 24 \quad \text{and } A_1 = 10 - 24$$

$$A_1 = -14$$

$$V_n = -14e^{-t} + 24e^{-2t} \quad \checkmark$$

LTSpice Time

* Critically damped Parallel RLC

- Happens when $\alpha^2 = \omega_0^2$, therefore $s_1 = s_2$

- Solution will be of the form,

$$V_n = e^{s_1 t} (A_1 t + A_2)$$


* Given:

$$L = 1 \text{ H}, R = 1 \Omega, C = \frac{1}{4} \text{ F}, V(0) = 5 \text{ V}, i_L(0) = -6 \text{ A}$$

$$\text{C.E.} = s^2 + 4s + 4$$

$$s_1 = s_2 = -2$$

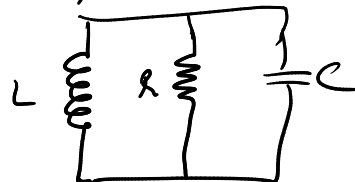Therefore, $V_n = e^{-2t} \overbrace{(A_1 t + A_2)}^{\text{Second}}$



At $t=0$

$$V(0) = e^{-2(0)} (A_1(0) + A_2)$$

$$V(0) = A_2 = 5V$$

* To find A_1 , we will find the derivative at $t=0$

$$\frac{dV}{dt} = A_1 \underline{e^{-2t}} - \underline{2A_1 t e^{-2t}} - 2A_2 \underline{e^{-2t}}$$

$$\frac{dV(0)}{dt} = A_1 - 2A_2$$

$$\frac{dV(0)}{dt} = -\frac{V(0)}{RC} - \frac{i(0)}{C} \quad \leftarrow \text{from Earlier}$$

* Therefore

$$A_1 - 2A_2 = \frac{-5}{1/4} - \frac{-6}{1/4}$$

$$A_1 - 10 = -20 - (-24)$$

$$A_1 = 14$$

$$V_n = e^{-2t} (14t + 5) \text{ V}$$

* Undamped Parallel RLC

When $\alpha^2 < \omega_0^2$ or when $L < 4R^2C$

* Roots will be complex conjugates

$$S_{1,2} = -\alpha \pm j\sqrt{\omega_0^2 - \alpha^2}$$

Where $j = \sqrt{-1}$

* We call $\sqrt{\omega_0^2 - \alpha^2}$ the damped resonant frequency ω_d

$$\Rightarrow S_{1,2} = -\alpha \pm j\omega_d$$

* The natural response is,

$$V_n = e^{-\alpha t} (A_1 e^{j\omega_d t} + A_2 e^{-j\omega_d t})$$

* Euler's Identity

$$e^{\pm j\omega_d t} = \cos(\omega_d t) \pm j \sin(\omega_d t)$$

$$V_n = e^{-\alpha t} \left[\underbrace{(A_1 + A_2)}_{B_1} \cos(\omega_d t) + j \underbrace{(A_1 - A_2)}_{B_2} \sin(\omega_d t) \right]$$

* Because A_1 and A_2 remain arbitrary we replace them with

$$V_n = e^{-\alpha t} (B_1 \cos(\omega_d t) + B_2 \sin(\omega_d t))$$

Where A_1 and A_2 must be complex conjugates so that

B_1 and B_2 are real numbers

* The underdamped response is oscillatory with a decaying magnitude

At $t=0$, $V_n(0) = B_1$ * Take derivative to find B_2

$$\frac{dV_n}{dt} = e^{-\alpha t} \left[(\omega_d B_2 - \alpha B_1) \cos(\omega_d t) - \underbrace{(\omega_d B_1 + \alpha B_2)}_0 \sin(\omega_d t) \right]$$

$$\frac{dV_n(0)}{dt} = \omega_d B_2 - \alpha B_1$$

* From earlier

$$\frac{dV(0)}{dt} = \frac{-V(0)}{RC} - \frac{i(0)}{C}$$

$$\Rightarrow \omega_d B_2 - \alpha B_1 = \frac{-V(0)}{RC} - \frac{i(0)}{C}$$

$$\Rightarrow \boxed{\omega_d B_2 = \alpha B_1 - \frac{V(0)}{RC} - \frac{i(0)}{C}}$$

* Example

Given
 $R = \frac{25}{3} \Omega$, $L = 0.1 \text{ H}$, $C = 1 \text{ mF}$, $V(0) = 10 \text{ V}$, $i(0) = -0.6 \text{ A}$

$$\alpha = \frac{1}{2RC} = 60 \quad \omega_0^2 = \frac{1}{LC} = 10^4$$

$\alpha^2 < \omega_0^2$ so underdamped circuit

* Find ω_d

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} = \sqrt{10^4 - 3.6 \times 10^3} = 80 \frac{\text{rad}}{\text{s}}$$

$$\therefore S_1 = -60 + j80$$

$$S_2 = -60 - j80$$

$$V_n = B_1 e^{-60t} \cos(80t) + B_2 e^{-60t} \sin(80t)$$

$$B_1 = V(0) = 10V$$

$$\omega B_2 = \alpha B_1 - \frac{V(0)}{RC} - \frac{i(0)}{C}$$

$$B_2 = 0$$

$$V_n = 10e^{-60t} \cos(80t) \text{ V}$$

HW Problems to be graded

Q1

Q2

Q8
