
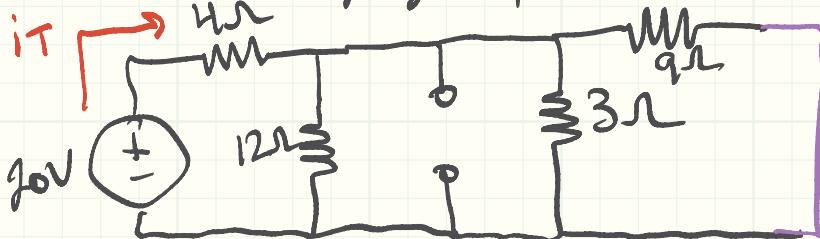


@ $t < 0$ applying superposition

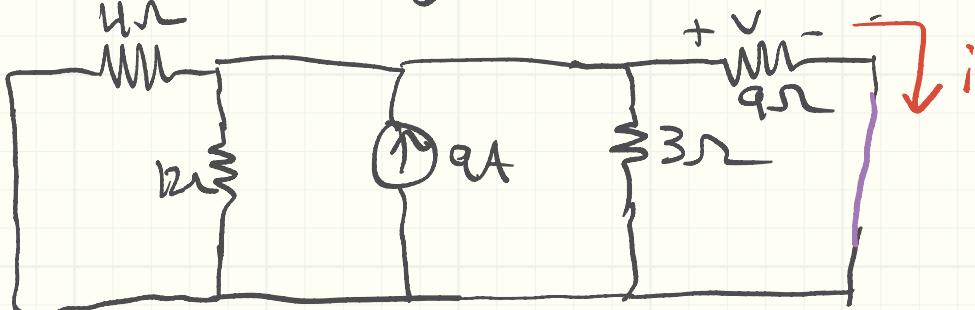

$$i_T = \frac{20}{(4 + 12 || 3 || 9)} = 3.39 \text{ A}$$


$$i_{9\Omega} = \frac{3 || 12}{3 || 12 + 9} (3.39) = 0.714 \text{ A}$$



$$i = \frac{12 || 4 || 3}{12 || 4 || 3 + 9} (9) = 1.28 \text{ A}$$

$$\Rightarrow i(0) = i_{9\Omega} + i = 0.714 + 1.28 = 1.994 \text{ A}$$

@ $t > 0$

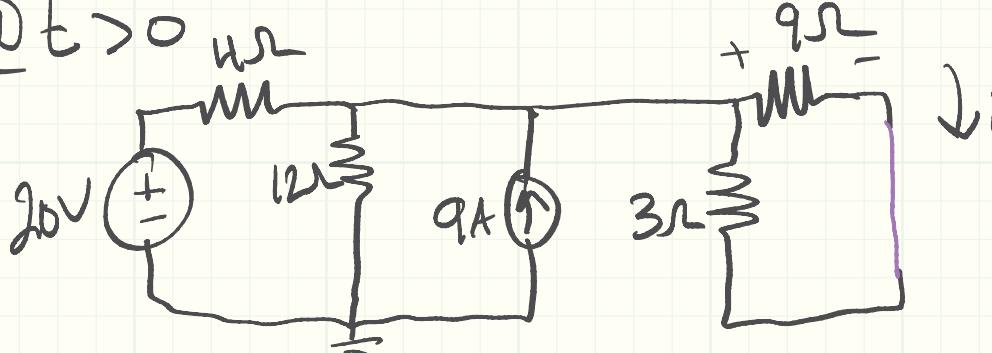

$$i(\infty) = 0 \text{ A} \text{ since } V_L(\infty) = 0$$


$$\Rightarrow i(t) = i_L(\infty) + [i_L(0) - i_L(\infty)] e^{-\frac{t}{\tau}}$$

$$R_{\text{eq}} = 9 + 3 = 12 \Omega$$

$$\tau = \frac{L}{R_{\text{eq}}} = \frac{12}{12} = \frac{1}{24}$$


$$i(t) = 1.994 e^{-24t} \text{ A}$$
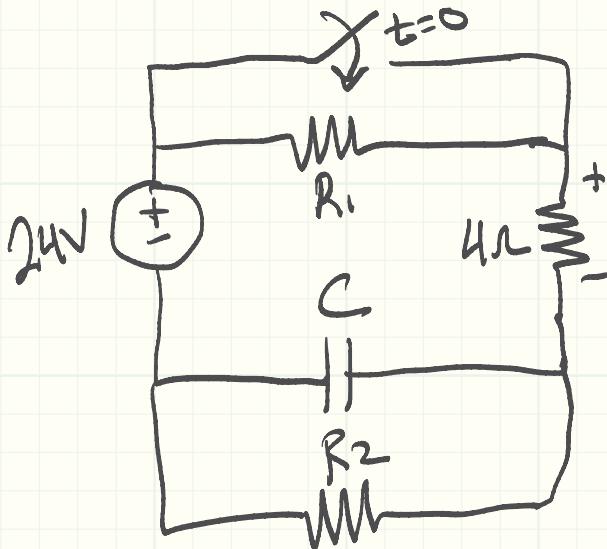
$$V(t) = 9 * i(t) = \boxed{17.946 e^{-24t} \text{ V}}$$



Given
 $V(t) = 8 + 4e^{-2t}$ V
 for $t > 0$
 Find R_1, R_2, C

@ $t < 0$

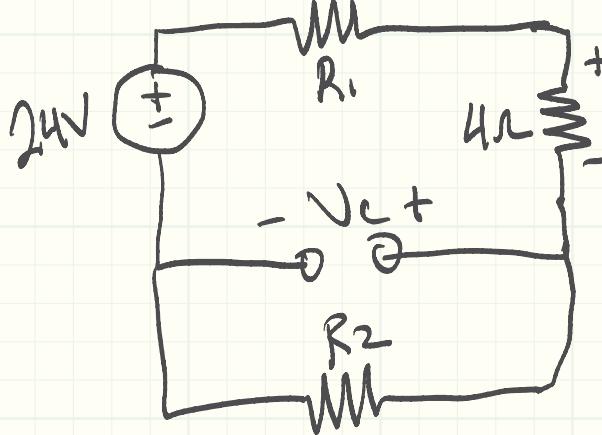


$$V_c(0) = -V(0) = -(-24)$$

$$V(0) = 8 + 4e^0 = 12 \text{ V}$$

$$V_c(0) = -12 + 24 = 12 \text{ V}$$

@ $t > 0$

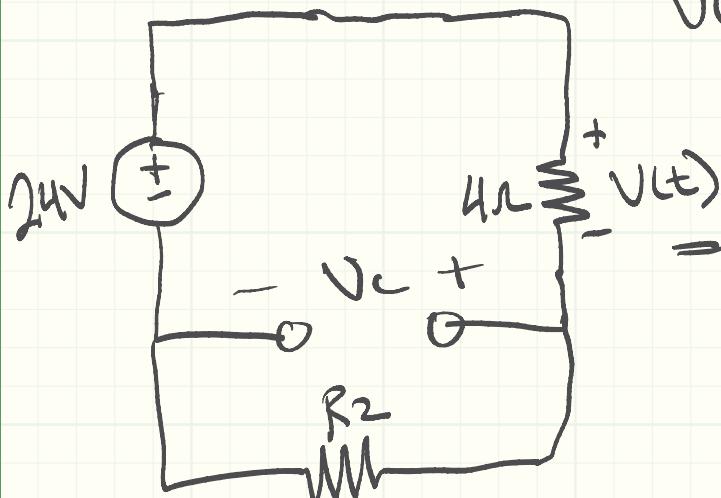

* R_1 is bypassed by short circuit


$$V(\infty) = 8 + 4e^{-\infty} = 8 \text{ V}$$

$$8 = \frac{4}{4+R_2} * 24$$

$$\Rightarrow 4+R_2 = \frac{4}{8} * 24$$

$$\Rightarrow R_2 = 8\Omega$$

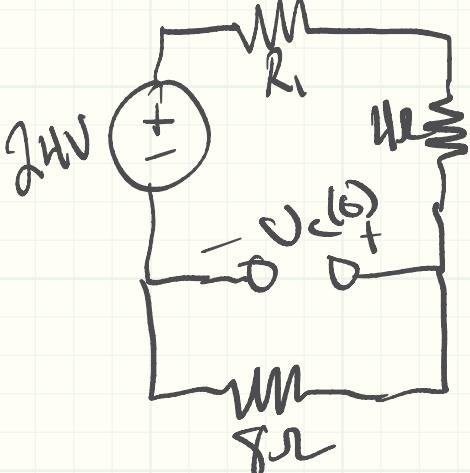*Now with R_2 , back to circuit for $t < 0$



$$V_c(0) = \frac{8}{8+4+R_1} * 24$$


$$\Rightarrow 12 = \frac{8}{12+R_1} * 24$$

$$\Rightarrow R_1 = 4\Omega$$

From $V(t) = 8 + 4e^{-2t}$

$$\bar{I} = \frac{1}{2} \Rightarrow R_{eq} C = \frac{1}{2}$$

$\underbrace{R_{eq}}$ for $t > 0$

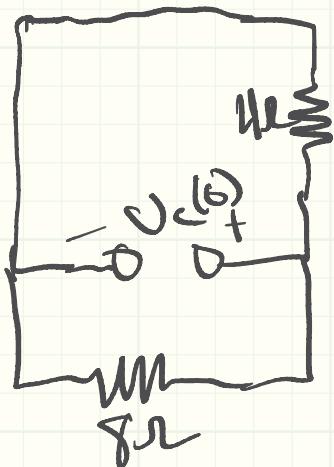


$$R_{eq} = 4 \parallel 8 = \frac{8}{3}\Omega$$

$$\bar{I} = \left(\frac{8}{3}\right)C = \frac{1}{2}$$


$$C = \frac{3}{16}$$

or
 $C = 187.5 \text{ mF}$

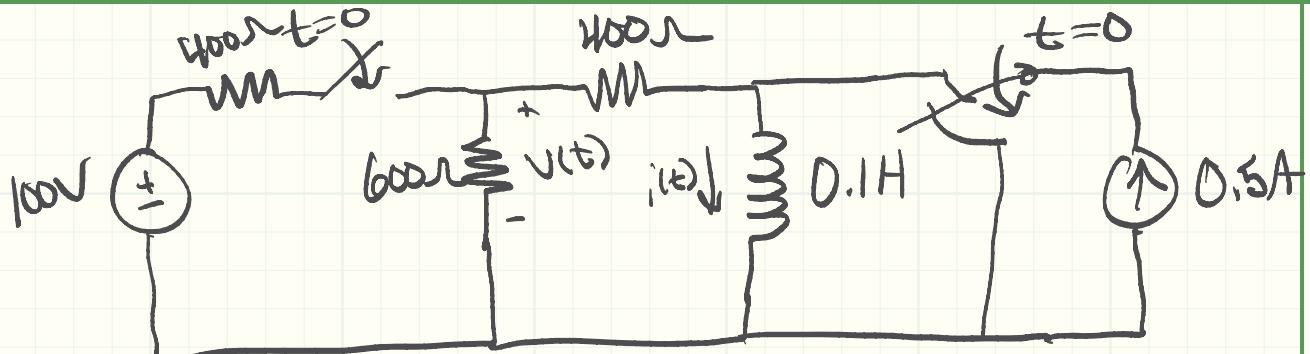


$\text{@ } t < 0$

$$i(0) = 0.5 \text{ A}$$

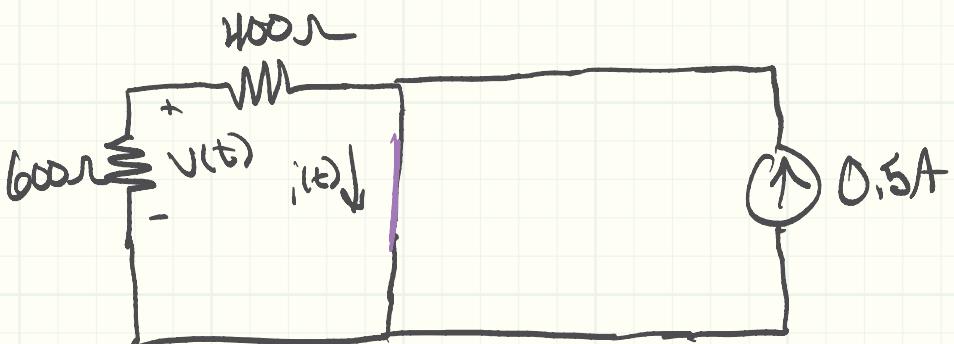

$t > 0$

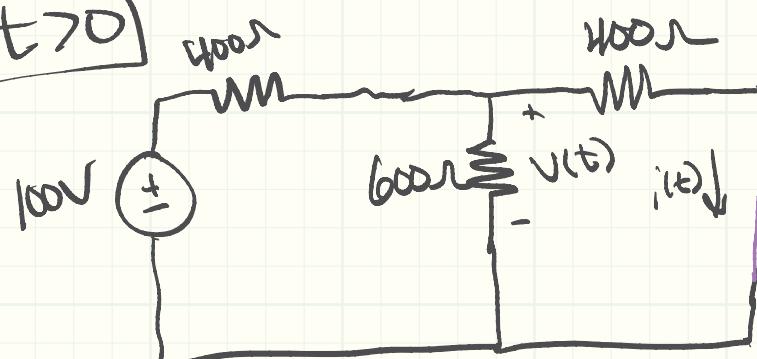


$$V(\infty) = \frac{600}{600+400} \times 100$$

$$V(\infty) = 37.5$$

$$i(\infty) = \frac{37.5}{400} = 93.75 \text{ mA}$$

Req

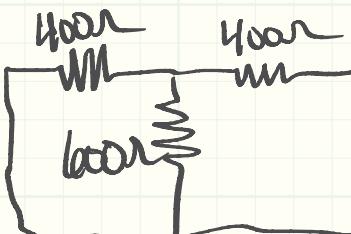


$$\text{Req} = 400 \parallel 600 + 400 = 640 \Omega$$

$$T = \frac{L}{\text{Req}} = \frac{0.1}{640} = \frac{1}{6400}$$

$$i(t) = 93.75 \times 10^{-3} + \left[0.5 - 93.75 \times 10^{-3} \right] e^{-6400t}$$

$$i(t) = 93.75 + 406.25 e^{-6400t} \text{ mA}$$

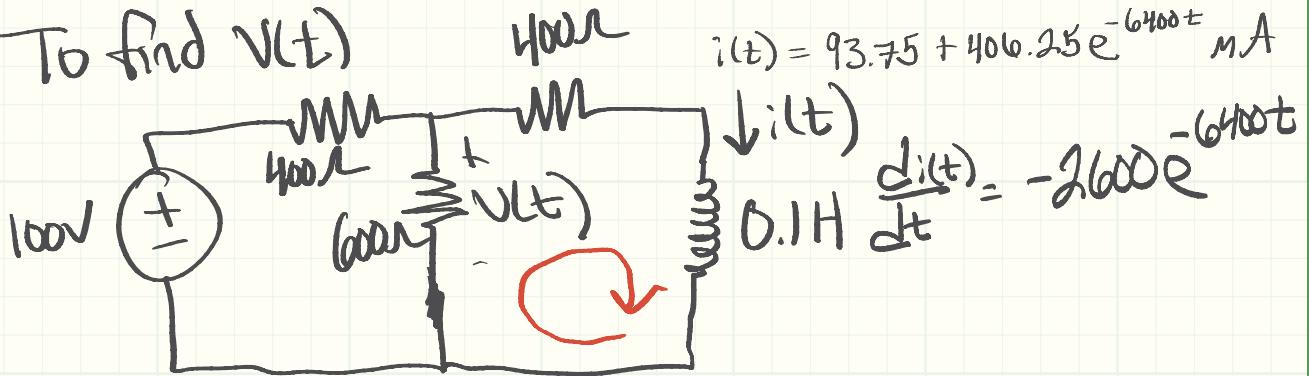To find $V(t)$ 

$$i(t) = 93.75 + 406.25 e^{-6400t} \text{ mA}$$

$$\frac{di(t)}{dt} = -2600 e^{-6400t}$$

$$V(t) = 400i(t) + 0.1 \frac{di(t)}{dt}$$



$$\Rightarrow V(t) = [37.5 + 162.5 e^{-6400t}]$$

$$+ [-260e^{-6400t}] \checkmark$$

$$V(t) = 37.5 - 97.5 e^{-6400t} \checkmark$$

P 8.3-19

7

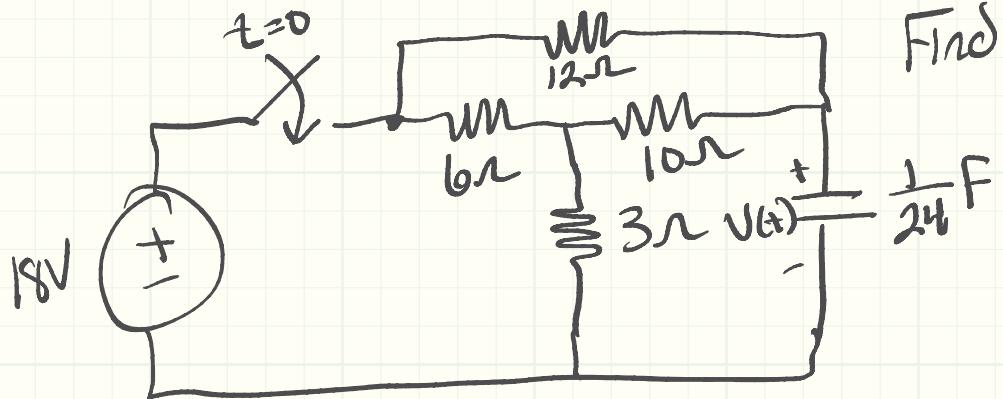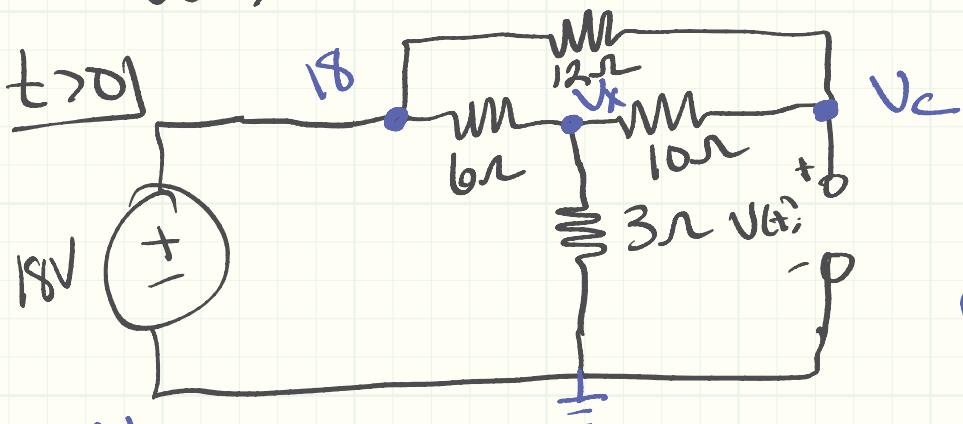Find $V(t)$ $t < 0$ $V_c(0) = 0 \text{ V}$ since no source is connected.

$$i_C = C \frac{dV_C}{dt}$$

 $\text{@ } V_x$

$$\frac{1}{6}(V_x - 18) + \frac{1}{3}(V_x - 0) + \frac{1}{10}(V_x - V_C) = 0$$

$$\left[\frac{1}{6} + \frac{1}{3} + \frac{1}{10} \right] V_x + \left[-\frac{1}{10} \right] V_C = 3$$

 $\text{@ } V_C$

$$\frac{1}{3}(V_C - 18) + \frac{1}{10}(V_C - V_x) = 0$$

$$\left[-\frac{1}{10} \right] V_x + \left[\frac{1}{12} + \frac{1}{10} \right] V_C = 1.5$$

Solving yields

$$V_x = 7V \quad V_C = 12V = V(\infty)$$