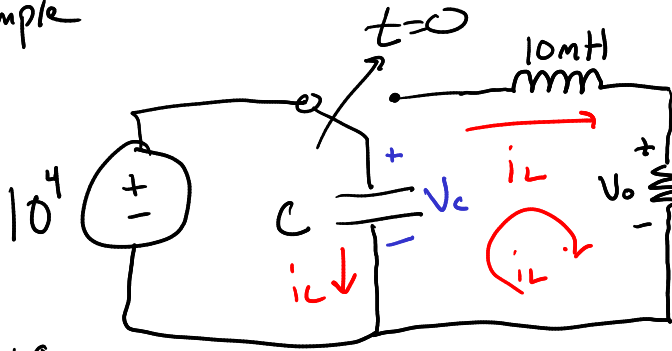


Lecture 6

Housekeeping: Exam is moved back 1 week

*Example

Stun Gun



Find $V_o(t)$ and select C so that the response is critically damped

For $t < 0$

$$V_C(0) = 10^4 \text{ V} \quad i_L(0) = 0 \text{ A}$$

$t > 0$ Mesh

$$-V_C + V_L + V_o = 0 \Rightarrow V_C = L \frac{di_L}{dt} + i_L R$$

Take the derivative

$$\frac{dV_C}{dt} = L \frac{d^2 i_L}{dt^2} + R \frac{di_L}{dt}$$

Substitute

Remember

$$i_C = C \frac{dV_C}{dt}$$

$$i_C = -i_L$$

\Rightarrow

$$i_C = LC \frac{d^2 i_L}{dt^2} + RC \frac{di_L}{dt}$$

$$\Rightarrow LC \frac{d^2 i_L}{dt^2} + RC \frac{di_L}{dt} + i_L = 0$$

Divide by LC

$$\frac{d^2 i_L}{dt^2} + \frac{R}{L} \frac{di_L}{dt} + \frac{1}{LC} i_L = 0$$

*Compare to $\frac{d^2 x(t)}{dt^2} + 2\alpha \frac{dx(t)}{dt} + \omega_0^2 x(t) = 0$

$$\omega_0^2 = \frac{1}{LC}$$

$$2\alpha = \frac{R}{L}$$

$$\therefore \alpha = \frac{R}{2L} = \frac{10^6}{2(10 \times 10^{-3})} = 50 \times 10^6$$

*For critical damping $\alpha^2 = \omega_0^2$

$$\alpha^2 = \frac{1}{LC} \Rightarrow C = \frac{1}{L\alpha^2} = \boxed{0.04 \text{ pF}}$$

$$i_L(t) = (A_1 t + A_2) e^{s_1 t}$$

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} \quad \circ$$

$$s_1 = -\alpha$$

* To find A_2 ,

$$i_L(0) = (A_1(0) + A_2) e^{-50 \times 10^6(0)}$$

$$\therefore i_L(0) = A_2 \Rightarrow A_2 = 0$$

* To obtain A_1 ,

$$\frac{di_L}{dt} = \frac{d}{dt} (A_1 t + A_2) e^{-50 \times 10^6 t}$$

$$\Rightarrow (A_1 t + A_2) (-50 \times 10^6) e^{-50 \times 10^6 t} + e^{-50 \times 10^6 t} A_1$$

plug in $t=0$

$$\frac{di_L(0)}{dt} = -50 \times 10^6 A_2 + A_1$$

$$A_2 = 0$$

$$\therefore \frac{di_L(0)}{dt} = A_1$$

* From Earlier

$$V_c = L \frac{di_L}{dt} + i_L R \Rightarrow L \frac{di_L}{dt} = V_c - i_L R$$

$$\Rightarrow \frac{di_L}{dt} = \frac{V_c - i_L R}{L}$$


$$\frac{di_L(0)}{dt} = \frac{V_c(0) - i_L(0) R}{L} = \frac{10^4}{10 \times 10^{-3}} = 1 \times 10^6 = A_1$$

$$R = 10^6$$

$$i_L(t) = 1 \times 10^6 t e^{-50 \times 10^6 t}$$


$$V_o = i_L(t) R \Rightarrow V_o(t) = (1 \times 10^{12}) t e^{-50 \times 10^6 t} \text{ V}$$

* Example

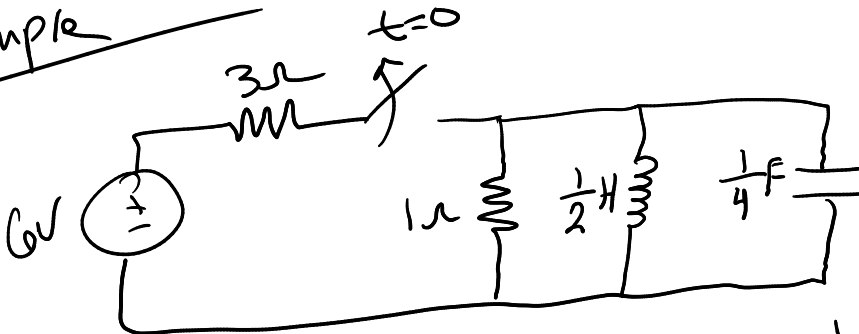

Determine and plot $i_L(t)$ assuming Steady State


For $t < 0$

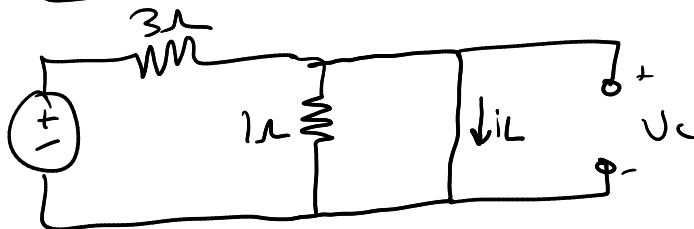

$$V_c(0) = 0 \checkmark$$

$$i_L(0) = \frac{6V}{3\Omega} = 2A$$

t > 0

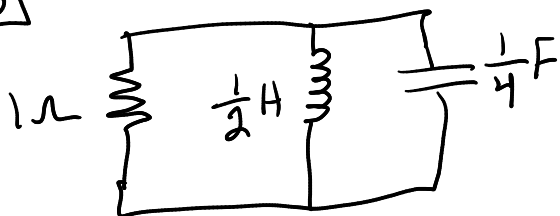

Parallel RLC Solution

$$\frac{d^2 i_L}{dt^2} + \frac{1}{RC} \frac{di_L}{dt} + \frac{1}{LC} i_L = 0$$

$$\alpha = \frac{1}{2RC} = \frac{1}{2(1)(\frac{1}{4})} = 2 \quad \omega_0^2 = \frac{1}{LC} = \frac{1}{(\frac{1}{2})(\frac{1}{4})} = 8$$

$\alpha^2 < \omega_0^2$ must underdamped circuit

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} = \sqrt{8 - 4} = 2 \frac{\text{rad}}{\text{sec}}$$

$$s_1 = -\alpha + j\omega_d = -2 + j2$$

$$s_2 = -\alpha - j\omega_d = -2 - j2$$

$$i_L(t) = e^{-\alpha t} (B_1 \cos(\omega_d t) + B_2 \sin(\omega_d t))$$

$$= e^{-2t} (B_1 \cos(2t) + B_2 \sin(2t))$$

$$i_L(0) = B_1 = 2 *$$

To find $\frac{di_L}{dt}$, use inductor voltage

$$\frac{di_L(0)}{dt} = 2B_2 - 2B_1$$

$$V_L = L \frac{di_L}{dt} \Rightarrow \frac{di_L}{dt} = \frac{V}{L}$$

$$\frac{di_L(0)}{dt} = 0 \quad V_L(0) = 0 \checkmark$$

$$\Rightarrow 2B_2 = 2B_1 \Rightarrow B_2 = 2$$

$$i_L(t) = e^{-2t} [2 \cos(2t) + 2 \sin(2t)] \text{ A}$$

* Forced Response

Total Response $x(t) = \text{natural} + \text{forced}$

$$\frac{d^2 x(t)}{dt^2} + 2\alpha \frac{dx(t)}{dt} + \omega_0^2 x(t) = f(t)$$


Forcing function

* The response to a forcing function will often be of the same form as the forcing function

Forced Responses

Forcing Function	Assumed Response
K	A
kt	$At + B$
kt^2	$At^2 + Bt + C$
$K \sin(\omega t)$	$A \sin(\omega t) + B \cos(\omega t)$
Ke^{-at}	Ae^{-at}

* Example

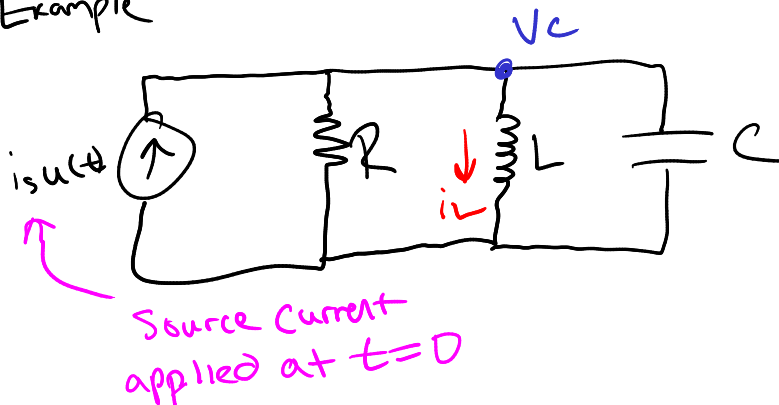

Given

$$i_s = 8e^{-2t} \text{ A}$$

$$R = 6 \Omega \quad C = \frac{1}{42} \text{ F}$$

$$L = 7 \text{ H}$$

Find the forced Response

KCL) $i_L + \frac{V_c}{R} + C \frac{dV_c}{dt} = i_s$

$$V_c = V_L = L \frac{di_L}{dt} \quad \frac{dV_c}{dt} = L \frac{d^2 i_L}{dt^2}$$

$$\Rightarrow i_L + \frac{L}{R} \frac{di_L}{dt} + LC \frac{d^2 i_L}{dt^2} = i_s$$

$$\Rightarrow \frac{d^2 i_L}{dt^2} + \frac{1}{RC} \frac{di_L}{dt} + \frac{1}{LC} i_L = \frac{i_s}{LC} \quad \text{Plug in numbers :)} \quad i_s = 8e^{-2t}$$

$$\Rightarrow \frac{d^2 i_L}{dt^2} + 7 \frac{di_L}{dt} + 6i_L = 48e^{-2t}$$

* Assumed Response $i_{Lf} = Be^{-2t}$

$$\frac{di_{Lf}}{dt} = -2Be^{-2t}$$

$$\frac{d^2 i_{Lf}}{dt^2} = 4Be^{-2t}$$

* Plug derivatives in!!

$$\Rightarrow 4Be^{-2t} - 14Be^{-2t} + 6Be^{-2t} = 48e^{-2t}$$

$$-4Be^{-2t} = 48e^{-2t}$$

$$B = -12 \text{ and } i_{Lf} = -12e^{-2t} \text{ A}$$

*Example

A circuit is described by

$$\frac{d^2 i}{dt^2} + 9 \frac{di}{dt} + 20i = 6i_s$$

where

$$i_s = 6 + 2t \text{ A}$$

Find the forced response i_F for $t > 0$

$$\frac{d^2 i_F}{dt^2} + 9 \frac{di_F}{dt} + 20i_F = 36 + 12t$$

Assumed Response

$$i_F = At + B$$

$$\frac{di_F}{dt} = A \quad \frac{d^2 i_F}{dt^2} = 0$$

$$9A + 20At + 20B = 36 + 12t$$

$$20A = 12 \Rightarrow A = \frac{12}{20} = 0.6$$

$$9A + 20B = 36 \Rightarrow 20B = 30.6 \Rightarrow B = 1.53$$

$$i_F = 0.6t + 1.53 \text{ A}$$